

Assessment -6


1) verilog code for mealy and moore in modelism

THEORY

Mealy machine's output depends on both the current state & the current input.

Output changes immediately when the input changes. Generally, it requires fewer states than Moore.

DIAGRAM

 

VERILOG CODE FOR MEALY FSM

```
module seq-mealy(y,i,clk,rst);
    output y;
    input i,clk,rst;
    reg y;
    reg [1:0] cs,ns;
    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;
    always @(cs or i)
    begin
        y = 1'b0;
        case (cs)
            S0 : begin
                if (i)
                    ns = S1;
            end
        end
    end
```

MEALY FSM TESTBENCH

```

else
ns = s0;
end
s1: begin
if(i)
ns = s1;
else
ns = s2;
end
s2: begin
if(i)
ns = s3;
else
ns = s0;
end
s3: begin
if(i)
ns = s1;
else begin
ns = s2;
y = 1'b1;
end
end
endcase
end

```

```

module seq-mealy-test;
wire y;
reg i, clk, rst;
seq-mealy f1(y, i, clk, rst);
always
#5 clk = ~clk;
initial
begin
i = 1; clk = 0; rst = 1;
#10 rst = 0;
#10 i = 0;
#10 i = 1;
#10 i = 0;
#10 i = 1;
#10 i = 0;
#50 $stop;
end
endmodule

```

```

// current state logic - sequential logic
always @ (posedge clk or posedge rst)
begin
if (rst)
cs <= s0;
else
cs <= ns;
end
endmodule

```

PROCEDURE

1. Open model SIM and create new project
2. Add verilog source files for both mealy & moore sequence detectors
3. Write testbench code
4. Simulate after compiling all files to check for errors.
5. Get output & graph.
6. Compare the timing of outputs between mealy & moore models.

CONCLUSION

Mealy machine responded faster since its output depends on both state & input, while the Moore machine gave more stable output based on only the state.

2) Design & implement 0101 sequence detector using Moore Machine


TOPIC : Moore machine

THEORY:

A moore state machine is a finite state machine (FSM) where the output is determined solely by its current state.

That means output changes only when the state changes usually on the next clock edge, making it more stable & predictable.

DIAGRAM

 

VERILOG

```
module seq-moore (y,i, clk, rst);
    output y;
    input i, clk, rst;
    reg y;
    reg [2:0] cs, ns;
    parameter S0 = 3'b000;
    parameter S1 = 3'b001;
    parameter S2 = 3'b010;
    parameter S3 = 3'b011;
    parameter S4 = 3'b100;
    always @(cs or i)
    begin
        case (cs)
            S0 : if (i)
                ns = S1;
            else
                ns = S0;
```

```

ns = S0;
s1: if(i)
ns = S1;
else
ns = S2;
s2: if(i)
ns = S3;
else
ns = S0;
s3: if(i)
ns = S1;
else
ns = S4;
s4: if(i)
ns = S3;
else
ns = S0;
endcase
end

```

// current state logic - sequential logic

always @(posedge clk or posedge rst)

begin

73

if (rst)

cs <= S0;

else

cs <= ns;

end

// output logic - combinational

logic

always @(cs)

begin

if (cs == S4)

y = 1'b1;

else

y = 1'b0;

end

endmodule


TESTBENCH

```
module seq_moore_test;  
  wire y;  
  reg i, clk, rst;  
  seq_moore f1 (y, i, clk, rst);  
  always  
  # 5 clk = ~clk;  
  initial  
  begin  
    i = 1; clk = 0; rst = 1;  
  
    # 10 rst = 0;  
    # 10 i = 0;  
    # 10 i = 1;  
    # 10 i = 0;  
    # 10 i = 1;  
    # 10 i = 0;  
    # 50 $stop;  
  end  
endmodule
```

O/P verified
Diff 05/05/2015

CONCLUSION

 Its output depends only on the current state, making it stable & easier to design compared to the mealy machine.



2. Write verilog code for asynchronous decade counter.

Theory

An asynchronous counter (also called a ripple counter) is a type of counter where the flip-flops are not clocked simultaneously, instead one flip flop triggers the next.

VERILOG

```
module async-decade-counter (  
    input clk,  
    input reset,  
    output reg [3:0] q  
);  
    always @(posedge clk or posedge reset)  
    begin  
        if (reset)  
            q <= 4'b0000;  
        else if (q == 4'b1001)  
            q <= 4'b0000;  
        else  
            q <= q+1;  
        end  
    endmodule
```

```
module async-decade-counter-tb;  
    reg clk;  
    reg reset;  
    wire [3:0] q;  
    async-decade-counter uut(  
        .clk (clk),  
        .reset (reset),  
        .q (q)  
    );  
    initial begin  
        clk = 0;  
        forever #5 clk = ~clk;  
    end
```

```
initial begin  
  reset = 1;
```

```
# 10;
```

```
  reset = 0;
```

```
# 200;
```

```
  reset = 1;
```

```
# 10;
```

```
  reset = 0;
```

```
# 100;
```

```
$stop;
```

```
end
```

```
initial begin
```

```
$monitor ("Time = %0t | reset = %b | Count = %b (%0.0d)",
```

```
$time, reset, q, q);
```

```
end
```

```
endmodule
```

CONCLUSION

The counter correctly counts from 0 to 9 and resets to 0, verifying the proper operation of a mod-10 asynchronous counter.

