

8:3 Priority Encoder

y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	0	1	X	0	0	1	1
0	0	0	0	0	1	X	X	0	1	0	1
0	0	0	0	1	X	X	X	0	1	1	1
0	0	0	1	X	X	X	X	1	0	0	1
0	0	1	X	X	X	X	X	1	0	1	1
0	1	X	X	X	X	X	X	1	1	0	1
1	X	X	X	X	X	X	X	1	1	1	1

- $a = y_7 \mid (y_6 \& \sim y_7) \mid (y_5 \& \sim y_6 \& \sim y_7) \mid (y_4 \& \sim y_5 \& \sim y_6 \& \sim y_7)$
- $b = y_7 \mid (y_6 \& \sim y_7) \mid (y_3 \& \sim y_4 \& \sim y_5 \& \sim y_6 \& \sim y_7) \mid (y_2 \& \sim y_3 \& \sim y_4 \& \sim y_5 \& \sim y_6 \& \sim y_7)$
- $c = y_7 \mid (y_5 \& \sim y_6 \& \sim y_7) \mid (y_3 \& \sim y_4 \& \sim y_5 \& \sim y_6 \& \sim y_7) \mid (y_1 \& \sim y_2 \& \sim y_3 \& \sim y_4 \& \sim y_5 \& \sim y_6 \& \sim y_7)$
- $\text{valid} = d = y_0 \mid y_1 \mid y_2 \mid y_3 \mid y_4 \mid y_5 \mid y_6 \mid y_7;$

8:3 Priority Encoder using Dataflow

```
module priority_encoder_8to3_df (  
    input [7:0] in,  
    output [2:0] out,  
    output valid);  
  
    assign out[2] = in[7] | (in[6] & ~in[7]) | (in[5] & ~in[6] & ~in[7]) | (in[4] & ~in[5]  
    & ~in[6] & ~in[7]);  
  
    assign out[1] = in[7] | (in[6] & ~in[7]) | (in[3] & ~in[4] & ~in[5] & ~in[6] &  
    ~in[7]) | (in[2] & ~in[3] & ~in[4] & ~in[5] & ~in[6] & ~in[7]);  
  
    assign out[0] = in[7] | (in[5] & ~in[6] & ~in[7]) | (in[3] & ~in[4] & ~in[5] &  
    ~in[6] & ~in[7]) | (in[1] & ~in[2] & ~in[3] & ~in[4] & ~in[5] & ~in[6] & ~in[7]);  
  
    assign valid = in[0] | in[1] | in[2] | in[3] | in[4] | in[5] | in[6] | in[7];  
  
endmodule
```

8:3 Priority Encoder using Dataflow

```
module priority_encoder_8to3_df (  
input [7:0] in,  
output [2:0] out,  
output valid);  
assign out = (in[7]) ? 3'b111 :  
    (in[6]) ? 3'b110 :  
    (in[5]) ? 3'b101 :  
    (in[4]) ? 3'b100 :  
    (in[3]) ? 3'b011 :  
    (in[2]) ? 3'b010 :  
    (in[1]) ? 3'b001 :  
    (in[0]) ? 3'b000 :  
    3'b000;  
assign valid = in[0] | in[1] | in[2] | in[3] | in[4] | in[5] | in[6] | in[7];  
endmodule
```

8:3 Priority Encoder Test Bench

```
module priority_encoder_8to3_df_tb;
reg [7:0] in;
wire [2:0] out;
wire      valid;
priority_encoder_8to3_df p (.in(in), .out(out), .valid(valid));
initial begin
in = 8'b00000000; #100;
in = 8'b00000001; #100;
in = 8'b00000010; #100;
in = 8'b00000100; #100;
in = 8'b00001000; #100;
in = 8'b00010000; #100;
in = 8'b00100000; #100;
in = 8'b01000000; #100;
in = 8'b10000000; #100;
in = 8'b11111111; #100;
in = 8'b00010010; #100;
$finish;
end
endmodule
```

Behavioral modeling

- Behavioral modeling represents digital circuits at a functional and algorithmic level.
- It is used mostly to describe sequential circuits, but can be used also to describe combinational circuits.
- **Behavioral** descriptions use the keyword **always** followed by a list of procedural assignment statements.
- The **target output** of procedural assignment statements must be of the **reg** data type. Contrary to the **wire** data type, where the target output of an assignment may be **continuously updated**.
- A **reg** data type **retains its value until a new value is assigned**.

Behavioral modeling

- Uses procedural blocks and procedural statements
- There are two types of procedural blocks in Verilog

1. The initial block

- ✧ Executes the enclosed statement(s) one time only

2. The always block

- ✧ Executes the enclosed statement(s) repeatedly until simulation terminates

- The body of the initial and always blocks is procedural
 - Can enclose one or more procedural statements
 - Procedural statements are surrounded by begin ... End
- Multiple procedural blocks can appear in any order inside a module and run in parallel inside the simulator

initial Statement

- Once executable only
- Execution starts at 0 simulation time
- Execution stops when the last statement is executed
- Parallel execution in case of multiple initial blocks
- Multiple statements inside an initial block need to be grouped with **begin and end statements**

Example:

```
module stimulus;  
reg x, y, a, b, m;  
initial  
m = 1'b0; // single statement; does not need to be grouped  
Initial  
begin  
#5 a = 1'b1; // multiple statements; need to be grouped  
#25 b = 1'b0;
```

```
end
```

```
Initial
```

```
begin
```

```
#10 x = 1'b0;
```

```
#25 y = 1'b1;
```

```
end
```

```
initial
```

```
#50 $finish;
```

```
endmodule
```

Simulation result

time	statement executed
0	m = 1'b0;
5	a = 1'b1;
10	x = 1'b0;
30	b = 1'b0;
35	y = 1'b1;
50	\$finish;

Example: cont.

- The three initial statements start to execute in parallel at time 0.
- If a delay #<delay> is seen before a statement, the statement is executed <delay> time units after the current simulation time.

always Statement

- Repeats continuously throughout the duration of simulation time
- Like initial block it is also concurrent in nature and starts at 0 simulation time
- Parallel execution in case of multiple always blocks
- A deadlock condition will be created if an always construct has no control for simulation time

always Construct

- The statements which come under the always construct constitute the always block.
- The always block starts at time 0, and keeps on executing all the simulation time.
- It works like an infinite loop.
- always blocks execute over and over again; in other words, as the name suggests, it executes always.

Structured Procedures: always statement

- Starts at time 0
- Execute the statements in a looping fashion
- Multiple always blocks, execute in parallel
All start at time 0

Syntax:

```
always @(sensitivity list)
begin
    // behavioral statements
end
```

"always" block example:

```
module and_or_gate (out, in1, in2, in3);
```

```
input  in1, in2, in3;
```

```
output out;
```

```
reg    out;
```

```
always @(in1 or in2 or in3)
```

```
begin
```

```
out = (in1 & in2) | in3;
```

```
end
```

```
endmodule
```

BASIC GATES (ALL GATES IN ONE PROGRAM)

```

module gates(a,b,c,d,e,f,g,h,i,j);
input a,b;
output c,d,e,f,g,h,i,j;
assign c=a&b;
assign d=a|b;
assign e=~a;
assign f=a;
assign g=~(a|b);
assign h=a^b;
assign i=~(a^b);
assign j=~(a&b);
endmodule

```

```

module gates(a,b,c,d,e,f,g,h,i,j);
input a,b;
output c,d,e,f,g,h,i,j;
reg c,d,e,f,g,h,i,j;
always @(a,b)
begin
c=a&b;
d=a|b;
e=~a;
f=a;
g=~(a|b);
h=a^b;
i=~(a^b);
j=~(a&b);
end
endmodule

```

```

module gates(a,b,c,d,e,f,g,h,i,j);
input a,b;
output c,d,e,f,g,h,i,j;
and (c,a,b);
or(d,a,b);
not(e,a);
buf(f,a);
nor(g,a,b);
xor(h,a,b);
xnor(i,a,b);
nand(j,a,b);
endmodule

```

Conditional statements

- **if-else** constructs
 - like C, except that instead of open and close brackets { ... } use keywords begin ... end to group multiple assignments associated with a given condition
 - begin ... end are not needed for single assignments
- **case** constructs
 - similar to C switch statements, selecting one of multiple options based on values of a single selection signal
- **for** (i = 0; i < 10; i = i + 1) statements
- **repeat** (count) statements // repeat statements “count” times
- **while** (abc) statements // repeat statements while abc “true” (non-0)

case statement

- The if-else statement provides the means for choosing an alternative based on the value of an expression.
- When there are many possible alternatives, the code based on this statement may become awkward to read.
- Instead, it is often possible to use the Verilog case statement which is defined as

case (expression)

alternative1: statement;

alternative2: statement; . . .

alternativej: statement;

[default: statement;]

endcase

Behavioral Modeling – Half Adder

//Half Adder : Behavioral description

```
module ha_beh (x,y,s,c);  
    input x,y;  
    output s,c;  
    reg s, c;  
    always @(x or y)  
        begin  
            s = x ^ y;  
            c = x & y;  
        end  
endmodule
```

Behavioral Modeling – Half Adder – using case

```
module half_adder(A, B, S, Cout);  
input A,B;  
output S, Cout;  
reg S, Cout;  
always @(A or B)  
begin  
    case (A | B)  
        2'b00: begin S = 0; Cout = 0; end  
        2'b01: begin S = 1; Cout = 0; end  
        2'b10: begin S = 1; Cout = 0; end  
        2'b11: begin S = 0; Cout = 1; end  
    endcase  
end  
endmodule
```

Behavioral Modeling – Half Subtractor

//Half Subtractor : Behavioral description

```
module half_sub_beh(diff,borr,a,b);  
input a,b;  
output diff,borr;  
reg diff,borr;  
always@(a or b)  
begin  
diff=a^b;  
borr=~a&b;  
end  
endmodule
```

Behavioral Modeling – Full Adder

```
module full_add_beh(sum,carry,a,b,c);  
input a,b,c;  
output sum,carry;  
reg sum,carry;  
wire w1,w2,w3;  
always@(a,b,c)  
begin  
w1=a^b;  
sum=w1^c;  
w2=a&b;  
w3=w1&c;  
carry=w2|w3;  
end  
endmodule
```

Behavioral Modeling 2:1 Mux

- The procedural assignment statements inside the **always** block are executed every time there is a change in any of the variable listed after the @ symbol. (Note that there is no “;” at the end of **always** statement)

//Behavioral description of 2-to-1-line multiplexer

```
module mux2x1_bh(A,B,select,OUT);
```

```
  input A,B,select;
```

```
  output OUT;
```

```
  reg OUT;
```

```
  always @(select or A or B)
```

```
  begin
```

```
    if (select == 0) OUT = A;
```

```
    else OUT = B;
```

```
  end
```

```
endmodule
```

2:1 Mux using conditional operator

```
module mux2to1 (w0, w1, s, f);  
  
input w0, w1, s;  
  
output reg f;  
  
always @(w0, w1, s)  
  
f = s ? w1 : w0;  
  
endmodule
```

Behavioral Modeling 4-to-1 multiplexer

//Behavioral description of 4-to-1 line mux

module mux4x1_bh (i0,i1,i2,i3,select,y);

input i0,i1,i2,i3;

input [1:0] select;

output y;

reg y;

always @(i0 or i1 or i2 or i3 or select)

case (select)

 2'b00: y = i0;

 2'b01: y = i1;

 2'b10: y = i2;

 2'b11: y = i3;

endcase

endmodule

Behavioral Modeling 4-to-1 multiplexer

- In 4-to-1 line multiplexer, the select input is defined as a 2-bit vector and output y is declared as a reg data.
- The always block has a sequential block enclosed between the keywords **case** and **endcase**.
- The block is executed whenever any of the inputs listed after the @ symbol changes in value.

// function modeled by its “behavior”

module MUX2 (A,B,C,D,S,Z1,Z2);

input A,B,C,D; //mux inputs

input [1:0] S; //mux select inputs

output Z; //mux output

always //evaluate block whenever there are changes in S,A,B,C,D

begin //if-else form

if (S == 2'b00) Z1 = A; //select input A for S=00

else if (S == 2'b01) Z1 = B; //select input B for S=01

else if (S == 2'b10) Z1 = C; //select input C for S=10

else if (S == 2'b11) Z1 = D; //select input D for S=11

else Z1 = x; //otherwise unknown output

end

//assign statement using the conditional operator (in lieu of always block)

assign Z2 = (S == 2'b00) ? A; //select A for S=00

(S == 2'b01) ? B; //select B for S=01

(S == 2'b10) ? C; //select C for S=10

(S == 2'b11) ? D; //select D for S=11

x; //otherwise default to x

endmodule

//equivalent case statement form

case (S)

2'b00: Z1 = A;

2'b01: Z1 = B;

2'b10: Z1 = C;

2'b11: Z1 = D;

default: Z1 = x;

endcase

Synthesis may insert latches
when defaults not specified.

Behavioral Modeling – 4:1 Mux

```
module mux4to1 (w0, w1, w2, w3, S, f);  
  input w0, w1, w2, w3;  
  input [1:0] S;  
  output reg f;
```

```
  always @(*)  
    if (S == 2'b00)  
      f = w0;  
    else if (S == 2'b01)  
      f = w1;  
    else if (S == 2'b10)  
      f = w2;  
    else  
      f = w3;
```

```
endmodule
```

```
module mux4to1 (W, S, f);  
  input [0:3] W;  
  input [1:0] S;  
  output reg f;
```

```
  always @(W, S)  
    if (S == 0)  
      f = W[0];  
    else if (S == 1)  
      f = W[1];  
    else if (S == 2)  
      f = W[2];  
    else  
      f = W[3];
```

```
endmodule
```

Behavioral Modeling – 4:1 Mux

```
module mux4to1 (W, S, f);  
  input [0:3] W;  
  input [1:0] S;  
  output reg f;  
  
  always @(W, S)  
    case (S)  
      0: f = W[0];  
      1: f = W[1];  
      2: f = W[2];  
      3: f = W[3];  
    endcase  
  
endmodule
```

```
module MUX4 (A,B,C,D,S0,S1,Z);  
  input A,B,C,D,S0,S1;  
  output Z;  
  wire Z1,Z2;  
  always  
    begin  
      if      ((S1 == 1'b0) && (S0 == 1'b0)) Z = A;  
      else if ((S1 == 1'b0) && (S0 == 1'b1)) Z = B;  
      else if ((S1 == 1'b1) && (S0 == 1'b0)) Z = C;  
      else                                         Z = D;  
    end  
  
endmodule
```

1:4 Demux Verilog Code

```
module demux_1_4(  
    input [1:0] sel,  
    input i,  
    output reg y0,y1,y2,y3);  
  
    always @(*)  
begin  
    case(sel)  
        2'h0: {y0,y1,y2,y3} = {i,3'b0};  
        2'h1: {y0,y1,y2,y3} = {1'b0,i,2'b0};  
        2'h2: {y0,y1,y2,y3} = {2'b0,i,1'b0};  
        2'h3: {y0,y1,y2,y3} = {3'b0,i};  
        default: $display("Invalid sel input");  
    endcase  
end  
endmodule
```

Testbench Code

```
module tb;
  reg [1:0] sel;
  reg i;
  wire y0,y1,y2,y3;
  demux_1_4 demux(sel, i, y0, y1, y2, y3);
  initial begin
    $monitor("sel = %b, i = %b -> y0 = %0b, y1 = %0b ,y2 = %0b, y3 = %0b", sel,i,
y0,y1,y2,y3);
    sel=2'b00; i=0; #1;
    sel=2'b00; i=1; #1;
    sel=2'b01; i=0; #1;
    sel=2'b01; i=1; #1;
    sel=2'b10; i=0; #1;
    sel=2'b10; i=1; #1;
    sel=2'b11; i=0; #1;
    sel=2'b11; i=1; #1;
  end
endmodule
```

Behavioral Modeling – 2:4 Decoder

```
module dec2to4 (W, En, Y);  
    input [1:0] W;  
    input En;  
    output reg [0:3] Y;  
  
    always @(W, En)  
        case ({En, W})  
            3'b100: Y = 4'b1000;  
            3'b101: Y = 4'b0100;  
            3'b110: Y = 4'b0010;  
            3'b111: Y = 4'b0001;  
            default: Y = 4'b0000;  
        endcase  
  
endmodule
```

```
module dec2to4 (W, En, Y);  
    input [1:0] W;  
    input En;  
    output reg [0:3] Y;  
  
    always @(W, En)  
    begin  
        if (En == 0)  
            Y = 4'b0000;  
        else  
            case (W)  
                0: Y = 4'b1000;  
                1: Y = 4'b0100;  
                2: Y = 4'b0010;  
                3: Y = 4'b0001;  
            endcase  
        end  
  
endmodule
```

Behavioral Modeling – 3:8 Decoder

```
module binary_decoder(D, y);  
    input [2:0] D;  
    output reg [7:0] y;  
    always@(D) begin  
        y = 0;  
        case(D)  
            3'b000: y[0] = 1'b1;  
            3'b001: y[1] = 1'b1;  
            3'b010: y[2] = 1'b1;  
            3'b011: y[3] = 1'b1;  
            3'b100: y[4] = 1'b1;  
            3'b101: y[5] = 1'b1;  
            3'b110: y[6] = 1'b1;  
            3'b111: y[7] = 1'b1;  
            default: y = 0;  
        endcase  
    end  
endmodule
```

Test-Bench 3:8 Decoder

```
module tb;
  reg [2:0] D;
  wire [7:0] y;
  binary_decoder bin_dec(D, y);
  initial
  begin
    $monitor("D = %b -> y = %0b", D, y);
    repeat(5) begin
      D=$random;
      #100;
    end
  end
endmodule
```


8:3 Priority Encoder using Behavioral

```
module priority_encoder_8to3 (  
    input [7:0] in,  
    output reg [2:0] out,  
    output reg valid);  
    always @(*)  
    begin  
        valid = 1'b1;  
        casex (in)  
            8'b1xxxxxxx: out = 3'b111;  
            8'b01xxxxxx: out = 3'b110;  
            8'b001xxxxx: out = 3'b101;  
            8'b0001xxxx: out = 3'b100;  
            8'b00001xxx: out = 3'b011;  
            8'b000001xx: out = 3'b010;  
            8'b0000001x: out = 3'b001;  
            8'b00000001: out = 3'b000;  
            default: begin  
                out = 3'b000;  
                valid = 1'b0;  
            end  
        endcase  
    end  
endmodule
```


Hierarchical code – 4:16 Decoder

```
module dec4to16 (W, En, Y);  
    input [3:0] W;  
    input En;  
    output [0:15] Y;  
    wire [0:3] M;  
  
    dec2to4 Dec1 (W[3:2], M[0:3], En);  
    dec2to4 Dec2 (W[1:0], Y[0:3], M[0]);  
    dec2to4 Dec3 (W[1:0], Y[4:7], M[1]);  
    dec2to4 Dec4 (W[1:0], Y[8:11], M[2]);  
    dec2to4 Dec5 (W[1:0], Y[12:15], M[3]);  
  
endmodule
```

Hierarchical code – 16:1 Mux

```
module mux16to1 (W, S, f);  
    input [0:15] W;  
    input [3:0] S;  
    output f;  
    wire [0:3] M;  
  
    mux4to1 Mux1 (W[0:3], S[1:0], M[0]);  
    mux4to1 Mux2 (W[4:7], S[1:0], M[1]);  
    mux4to1 Mux3 (W[8:11], S[1:0], M[2]);  
    mux4to1 Mux4 (W[12:15], S[1:0], M[3]);  
    mux4to1 Mux5 (M[0:3], S[3:2], f);  
  
endmodule
```

Example

 

```
module f_g (x, y, z, f, g);  
  input x, y, z;  
  output f, g;  
  wire k;  
  
  assign k = y ^ z;  
  assign g = k ^ x;  
  assign f = (~k & z) | (k & x);  
  
endmodule
```

Consider the circuit shown in Figure 2.72. It includes two copies of the 2-to-1 multiplexer circuit from Figure 2.33, and the adder circuit from Figure 2.12. If the multiplexers' select input $m = 0$, then this circuit produces the sum $S = a + b$. But if $m = 1$, then the circuit produces $S = c + d$. By using multiplexers, we are able to *share* one adder for generating the two different sums $a + b$ and $c + d$. Sharing a subcircuit for multiple purposes is commonly-used in practice, although usually with larger subcircuits than our one-bit adder. Write Verilog code for the circuit in Figure 2.72. Use the hierarchical style of Verilog code illustrated in Figure 2.47, including two instances of a Verilog module for the 2-to-1 multiplexer subcircuit, and one instance of the adder subcircuit.

 


Figure 2.72 The circuit for Example 2.30.

Example

 


Figure 2.72 The circuit for Example 2.30.

```

module shared (a, b, c, d, m, s1, s0);
    input a, b, c, d, m;
    output s1, s0;
    wire w1, w2;
    mux2to1 U1 (a, c, m, w1);
    mux2to1 U2 (b, d, m, w2);
    adder U3 (w1, w2, s1, s0);
endmodule

```

```

module mux2to1 (x1, x2, s, f);
    input x1, x2, s;
    output f;
    assign f = (~s & x1) | (s & x2);
endmodule

module adder (a, b, s1, s0);
    input a, b;
    output s1, s0;
    assign s1 = a & b;
    assign s0 = a ^ b;
endmodule

```