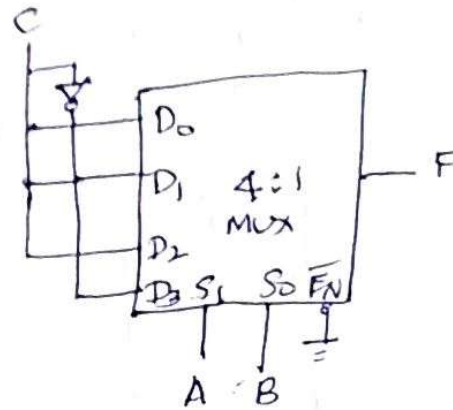


Method 2:

	$\bar{C}$	C	
C	0	①	D_0
C	2	③	D_1
C	4	⑤	D_2
$\bar{C}$	⑥	7	D_3

(a) Implementation table



(b) Multiplexer Implementation

- * In the previous (method 1) multiplexer implementation two least significant variables, i.e., B and C are connected to the select lines of the multiplexer.
- * The multiplexer implementation is also possible by connecting most significant variables i.e., A and B (in method 2) to the select lines of the multiplexer.
- * The procedure is also same which is explained below:
 - * Here, implementation table consists of two columns. The first ~~column~~ ^{row} lists all the minterms where least significant variable is complemented ($\bar{C}$ in this case), and the second ~~row~~ ^{column} lists all the minterms with least significant variable is uncomplemented (C in this case).
 - * The minterms given in the function are circled and then each row is inspected separately as follows:
 - If the two minterms in a row are not circled, 0 is applied to corresponding multiplexer input.

- If the two minterms in a row are circled, 1 is applied to corresponding multiplexer input.
- If the minterm in the column 1 is circled, least significant variable is complemented ($\bar{C}$ in this case) and applied to the corresponding multiplexer input.
- If the minterm in the column 2 is circled, least significant variable (C in this case) is applied to the corresponding multiplexer input.

1. Implement the following using 16×1 , 8×1 , 4×1 MUX.

$$F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$$


Decimal Value	A	B	C	D	F
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

Case 1: 16×1

$$\therefore 2^4 = 16$$

$n=4 \Rightarrow 4$ select lines

Here, No. of select lines = No. of Variables

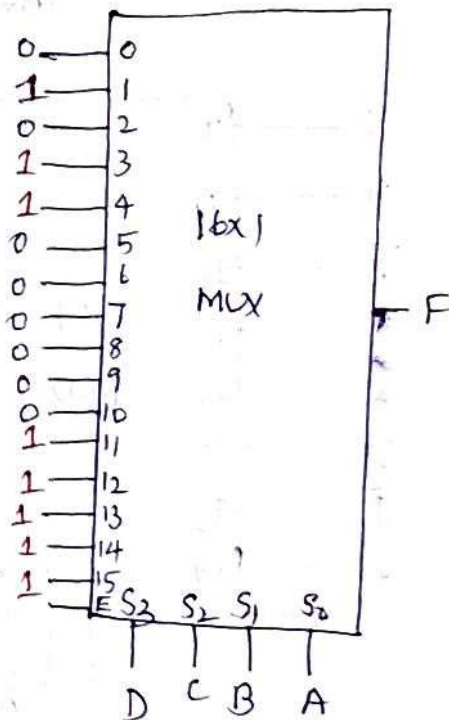

Case 2: 8x1 MUX

8 to 1 MUX $\Rightarrow 2^3 = 8$, $n=3$ data if select lines = 3


Since select lines are of variables of input
 $\therefore$ Remaining 1 variable will be input variable
 and the other 2 will be relation variables.
 $A, B, C \rightarrow$ select lines, $D \rightarrow$ will be mapped as input

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
$\bar{D}$	0	2	5	6	7	8	9	10
D	1	3	4	11	12	13	14	15

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
$\bar{D}$	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
D	D	D	$\bar{D}$	0	0	D	1	1

~~000~~

$D \cdot \bar{D} = 1$

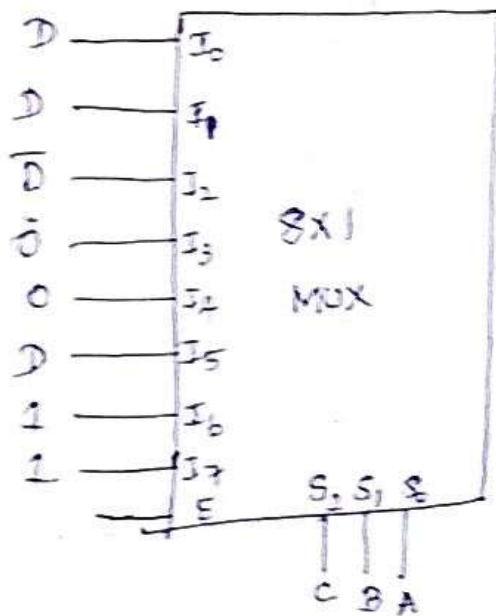

Q. 2) 10/2

Case 3: 4 x 1 MUX

Method 1:

$4 \times 1 \text{ MUX} = 2^2 = 4$, $\downarrow$ 2 select lines

No. of select lines $\neq$ No. of variables of input

$\therefore$ 2 variables for select lines & 2 variables for input variables.

Here, A, B $\rightarrow$ Input variables
C, D $\rightarrow$ Select lines

	I_0	I_1	I_2	I_3
$\bar{A}\bar{B}(00)$	0	①	2	③
$\bar{A}B(01)$	④	5	6	7
$A\bar{B}(10)$	8	9	10	⑪
$AB(11)$	⑫	⑬	⑭	⑮
	$\downarrow B$	$A \oplus B$	AB	$A + B$

$I_3 \rightarrow \bar{A}\bar{B} + \bar{A}B + AB$

$\Rightarrow \bar{B}(A + \bar{A}) + AB$


$\Rightarrow \bar{B} + AB$

$\Rightarrow \bar{B} + A$

$\therefore A + \bar{A}B = A + B$

$\Rightarrow \bar{A}B + AB \downarrow$

$\Rightarrow B(A + \bar{A}) = B$

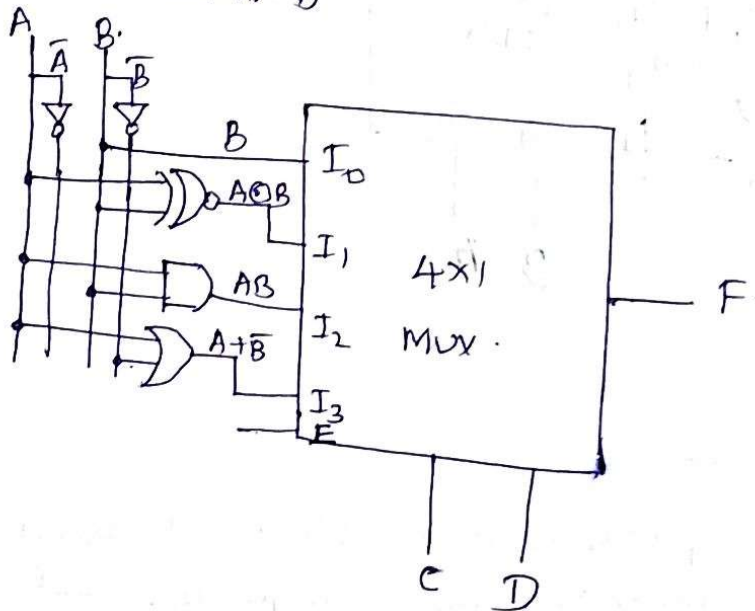


Method 2:

Here, $C, D \rightarrow$ Input variables
 $A, B \rightarrow$ Select lines

	I_0	I_1	I_2	I_3
$\bar{C}\bar{D}(00)$	0	④	8	⑫
$\bar{C}D(01)$	①	5	9	⑬
$C\bar{D}(10)$	2	6	10	⑭
$CD(11)$	③	7	⑪	⑮
	D	$\bar{C}\bar{D}$	CD	1

$$I_0 = \bar{C}D + CD$$
$$= D(C + \bar{C}) = D$$

$I_1 =$

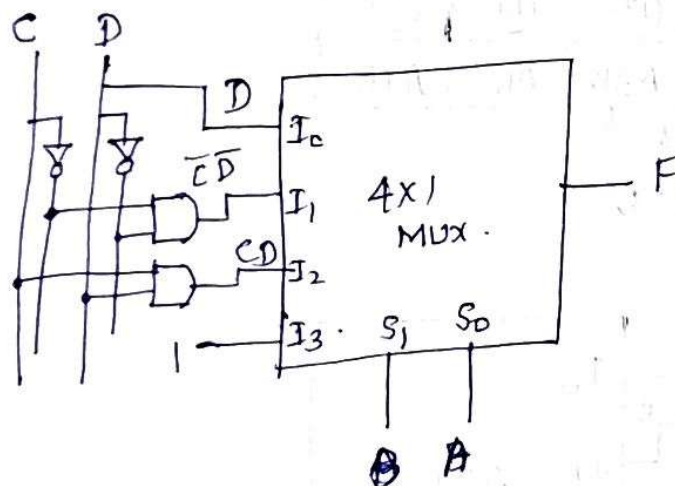

2.2.9 Demultiplexer:

* A demultiplexer is a combinational circuit that receives information on a single line and transmits this information on one of 2^n possible output lines.

* The selection of specific output line is controlled by the values of n selection lines.

* Fig. shows 1:4 demultiplexer.

Enable	S_1	S_0	D_{in}	Y_0	Y_1	Y_2	Y_3
0	x	x	x	0	0	0	0
1	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1

Table: Function table for 1:4 demultiplexer

* The single input variable D_{in} has a path to all four outputs, but the input information is directed to only one of the output lines.

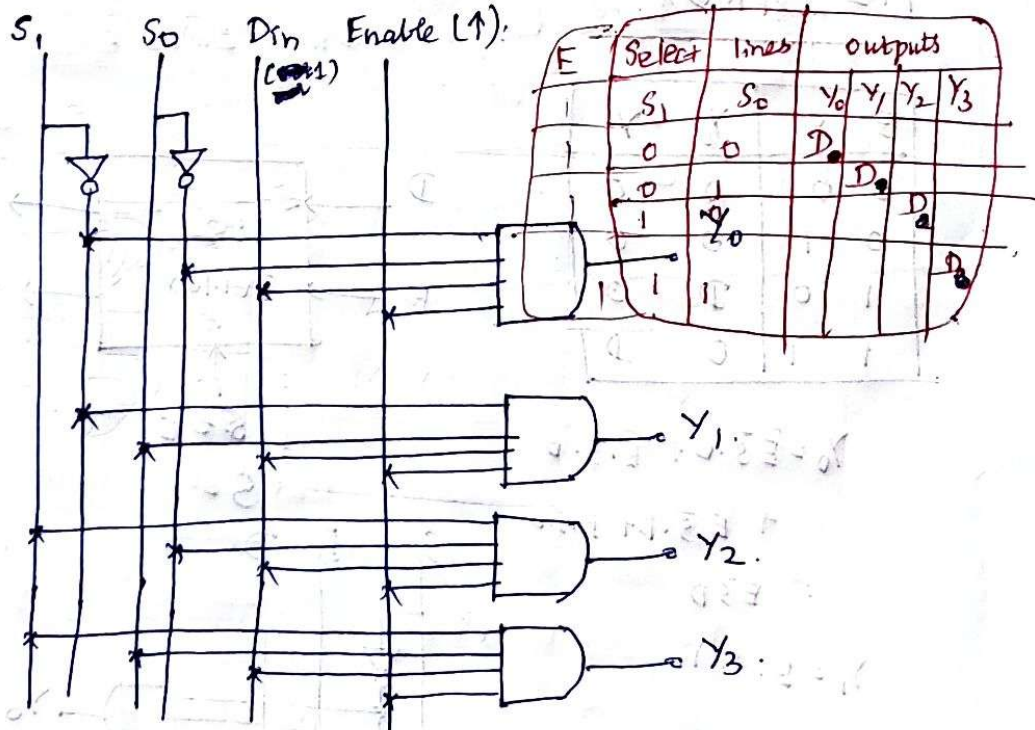


Fig: Logic diagram


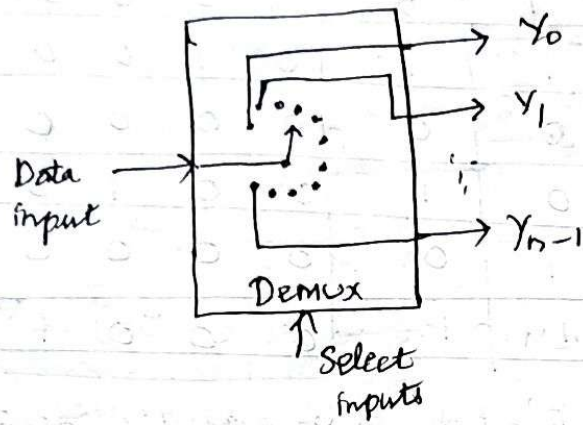
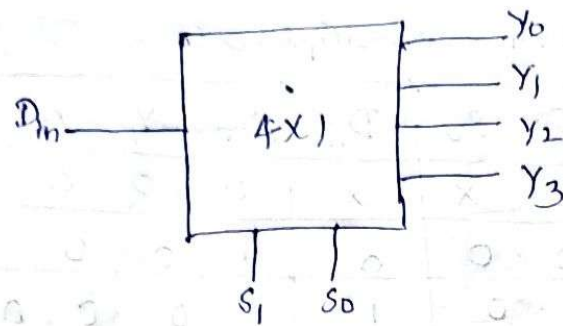


Fig: Functional diagram of a general demultiplexer

1:2 DEMUX:

E	S	Y_0	Y_1
0	0	0	0
0	1	0	0
1	0	D	0
1	1	0	D

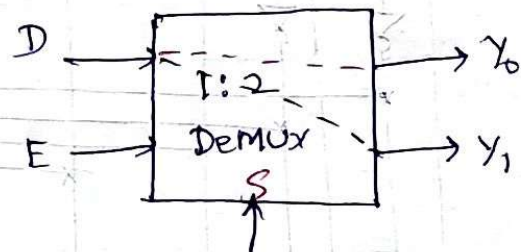


$$Y_0 = \bar{E}\bar{S} \cdot 0 + \bar{E}S \cdot 0 + E\bar{S} \cdot D + ES \cdot 0$$

$$= E\bar{S}D$$

$$Y_1 = E \cdot S \cdot D$$

$$S=0$$

$$S=1$$

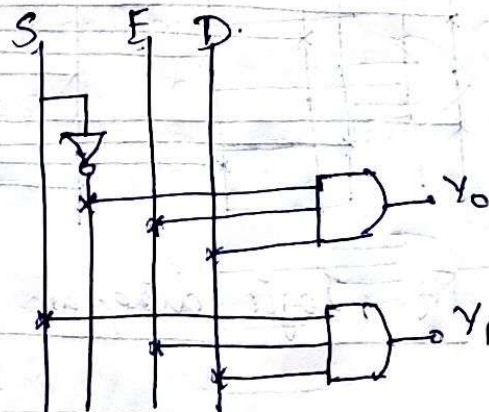

12.9) Implementing Boolean function using DeMux:


1. $f(A, B, C) = \sum m(0, 2, 4, 6)$. using **1:8 Mux**.

No. of input variables = 3 = No. of select lines


$1:2^n$
 $1:2^3 = 1:8 \Rightarrow n=3$. [1:8, 3 selection lines]

	S_2	S_1	S_0	Y
	A	B	C	f
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

S_2	S_1	S_0	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	0	1	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0

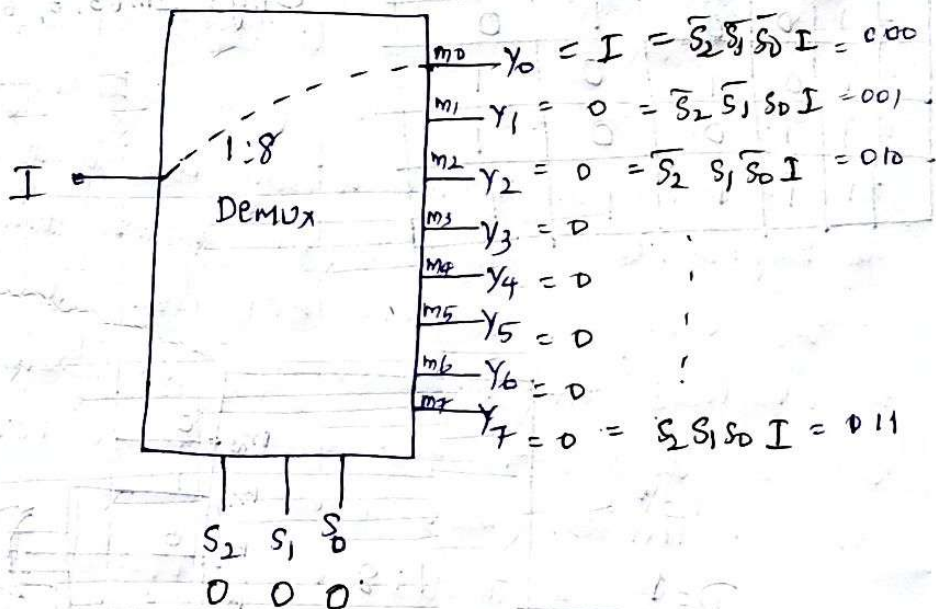

$$f = \sum m(0, 2, 4, 6)$$

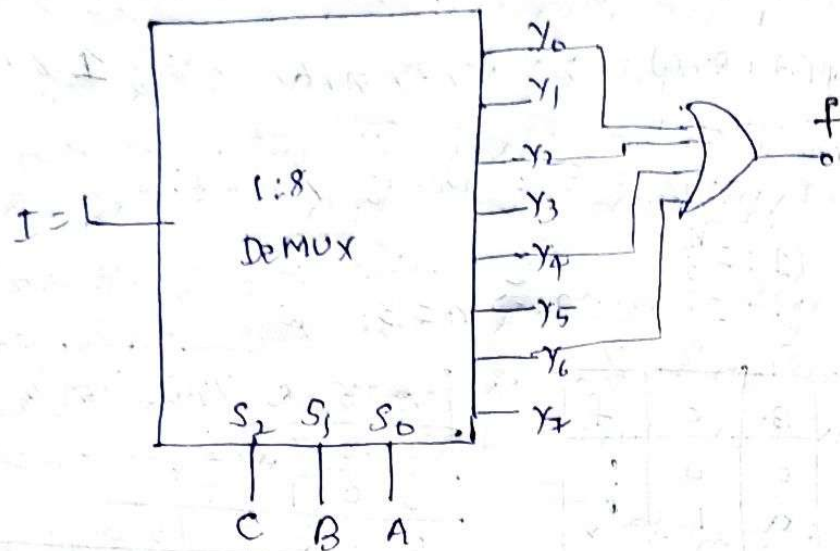

2. Implement full-adder using Demux:


	A	B	C_{in}	Sum	Carry
0	0	0	0	0	0
1	0	0	1	1	0
2	0	1	0	1	0
3	0	1	1	0	1
4	1	0	0	1	0
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1

$$1:2^n \Rightarrow 1:2^3 \Rightarrow n=3$$

3 select lines

$$\text{Sum} = \sum m(1, 2, 4, 7)$$

$$\text{Carry} = \sum m(3, 5, 6, 7)$$

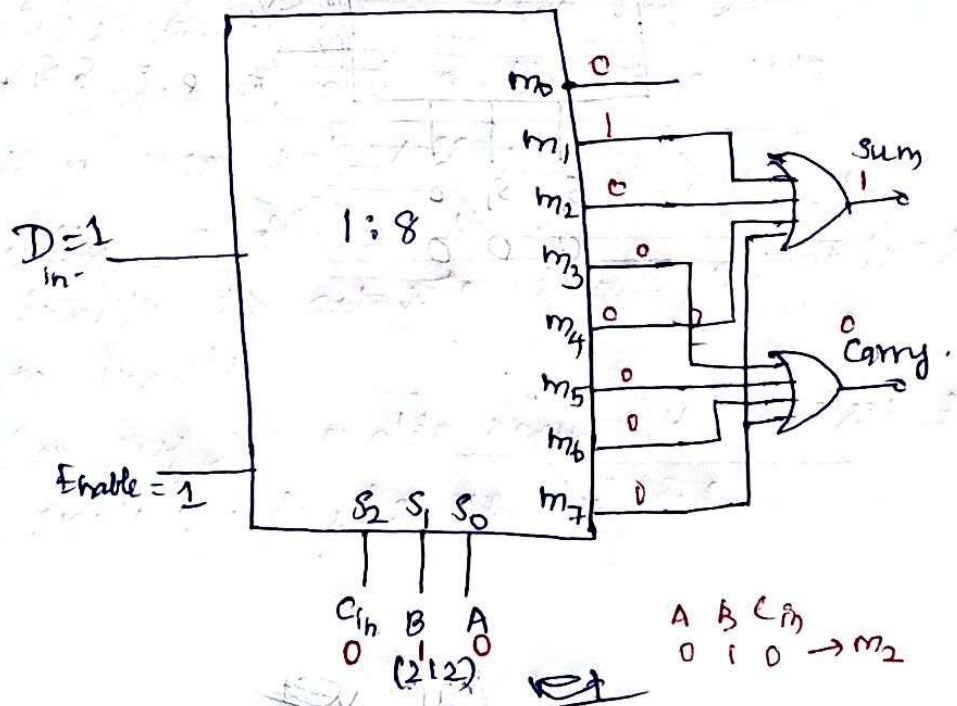


Implement full-subtractor using Demux

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = \sum m(1, 2, 4, 7)$$

$$Bout = \sum m(1, 2, 3, 7)$$

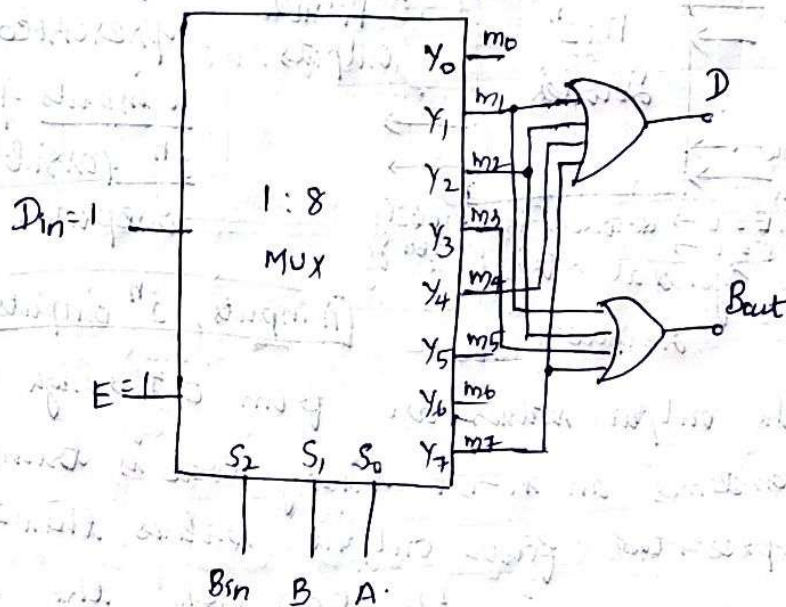

Decoders:

* A decoder is a multiple-input, multiple-output logic circuit which converts coded inputs into coded outputs, where the input and output codes are different. The input code generally has few bits than the output code.

* Each input code word produces a different output code word, i.e., there is one-to-one mapping from input code words into output code words.

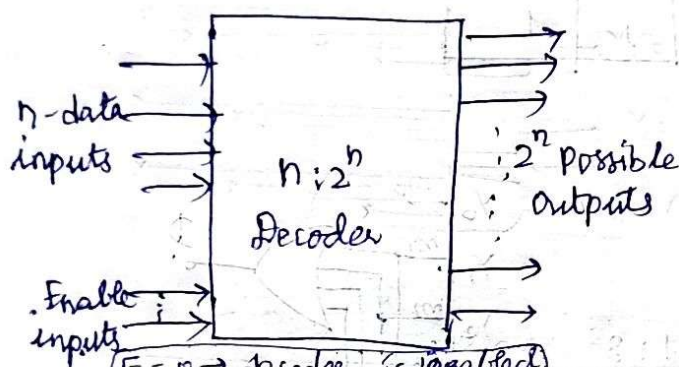


Fig: General structure of Decoder

* From the fig. the encoded information is presented as n inputs producing 2^n possible outputs.

n inputs, 2^n outputs with $E=1$


- * The output values are from 0 through $2^n - 1$.
- * Sometimes an n -bit binary code is truncated to represent fewer output values than 2^n .
- * For example, in the BCD code, the 4-bit combinations 0000 through 1001 represent the decimal digits 0-9, and combinations 1010 through 1111 are not used.

* Usually, a decoder is provided with enable inputs to activate decoded output based on data inputs.

* When any one enable input is unasserted, all outputs of decoder are disabled.

2 to 4 decoder: (Binary decoder)

E	A	B	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

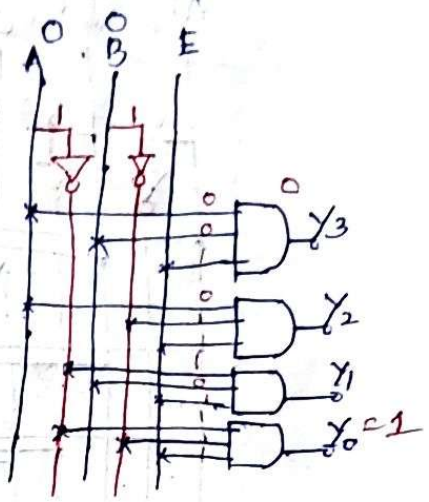

$$Y_3 = AB, Y_2 = A\bar{B}, Y_1 = \bar{A}B, Y_0 = \bar{A}\bar{B}$$

3 to 8 decoder:

n inputs, 2^n outputs with $E=1$, no select lines


$$n=3, 2^n=8 \text{ outputs, } E=1$$

E	A	B	C	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

$$Y_7 = ABC, Y_6 = AB\bar{C}, Y_5 = A\bar{B}C, Y_4 = A\bar{B}\bar{C}$$

$$Y_3 = \bar{A}BC, Y_2 = \bar{A}\bar{B}\bar{C}, Y_1 = \bar{A}\bar{B}C, Y_0 = \bar{A}\bar{B}\bar{C}$$

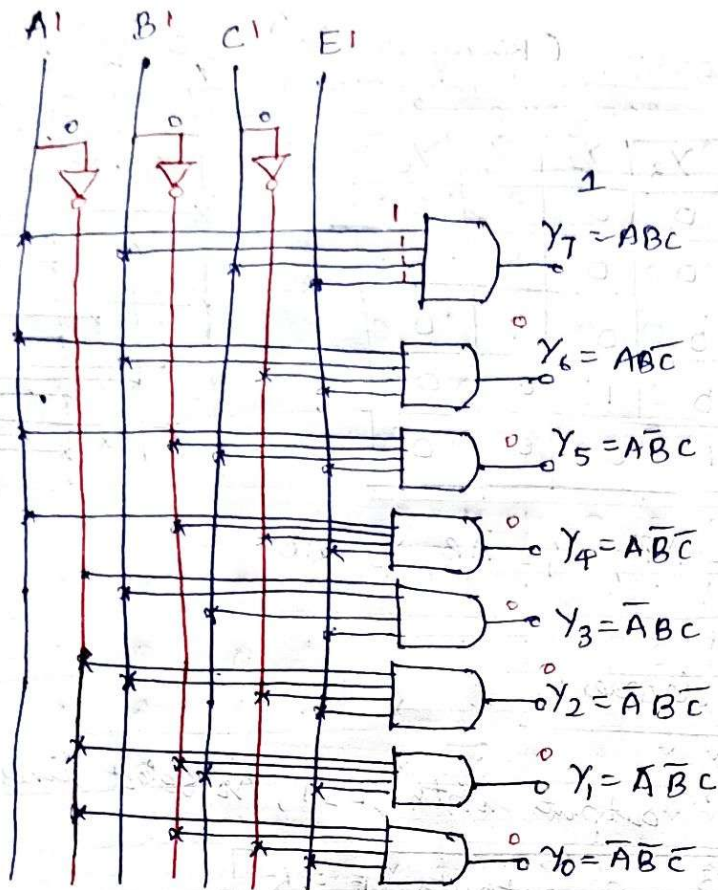Binary decoder: A decoder which has an n -bit binary input code and a one activated output out of 2^n output code is called Binary decoder. It is used when it is necessary to activate exactly one of 2^n outputs based on an n -bit input value.



2.2.10.3


BCD to 7-segment Display Decoder:

* BCD is 4 bits, $[0000 - 1001] \rightarrow$ Valid BCDs
 $[1010 - 1111] \rightarrow$ Invalid BCD.

* 10 in BCD is,
 $\downarrow \quad \downarrow$
 $0001 \quad 0000$


* The total number of segments to display BCD numbers from 0 to 9 is 7 segments [a, b, c, d, e, f, g].

* The seven segments are given below,

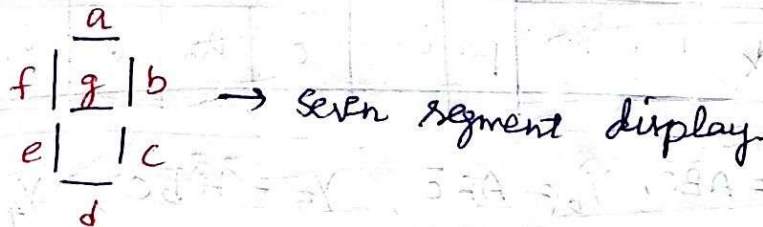

Digit	Segments Activated	Display
0	a, b, c, d, e, f	

1	b, c	b c
2	a, b, d, e, g	$\frac{a}{2}$ b e d
3	a, b, c, d, g	$\frac{a}{2}$ b c d
4	b, c, f, g	f b g c
5	a, c, d, f, g	$\frac{a}{2}$ f g c d
6	a, c, d, e, f, g	$\frac{a}{2}$ f e g c d
7	a, b, c	$\frac{a}{2}$ b c
8	a, b, c, d, e, f, g	$\frac{a}{2}$ f b e g c d
9	a, b, c, d, f, g	$\frac{a}{2}$ f b g c d
10-15	X X X X X X X	Don't care conditions.

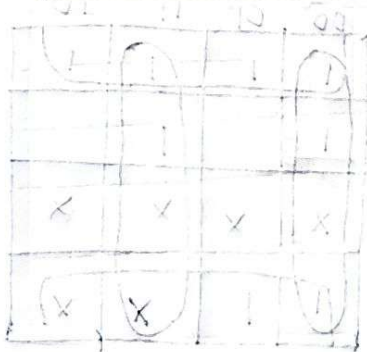

$a + b + c + d = 1$



$a + b + c + d = 1$

Digit	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
10	1	0	1	0	X	X	X	X	X	X	X
11	1	0	1	1	X	X	X	X	X	X	X
12	1	1	0	0	X	X	X	X	X	X	X
13	1	1	0	1	X	X	X	X	X	X	X
14	1	1	1	0	X	X	X	X	X	X	X
15	1	1	1	1	X	X	X	X	X	X	X

Table: Truth table for BCD to 7-segment decoder

For a






AB \ CD	00	01	11	10
00	1	0	1	1
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$a = A + C + BD + \bar{B}\bar{D}$$

For b

AB \ CD	00	01	11	10
00	1	1	1	1
01	1		1	
11	X	X	X	X
10	1	1	X	X

$$b = \bar{B} + \bar{C}\bar{D} + CD$$

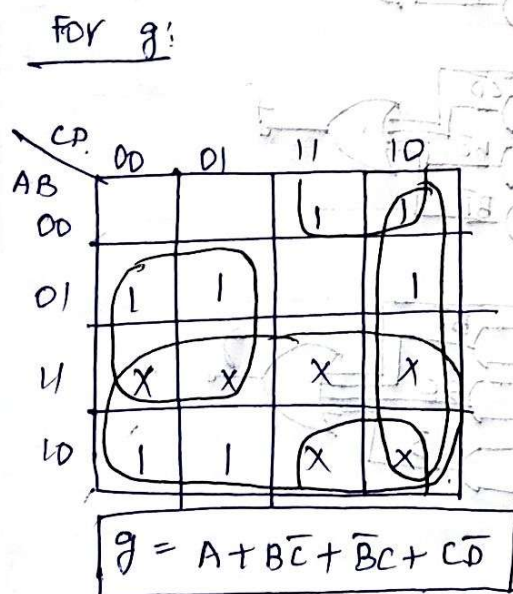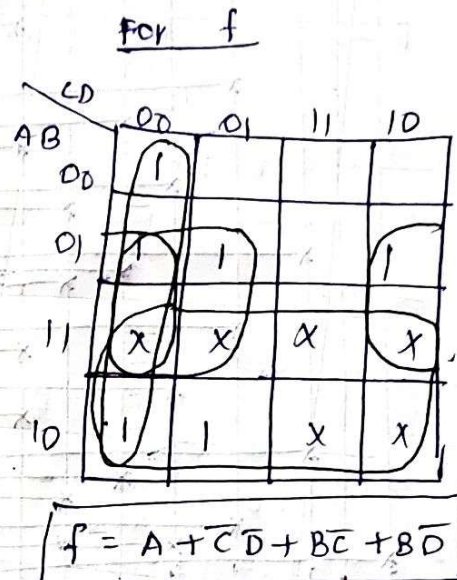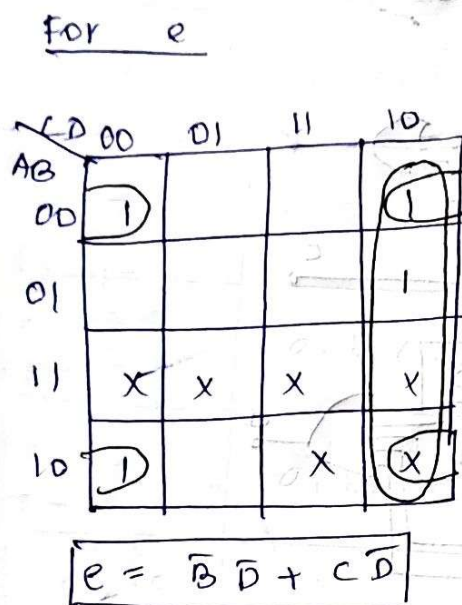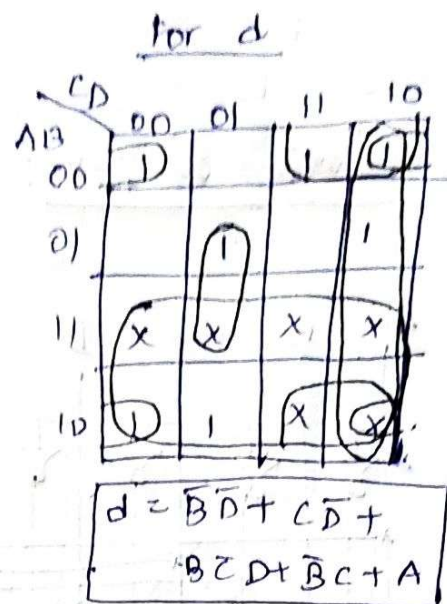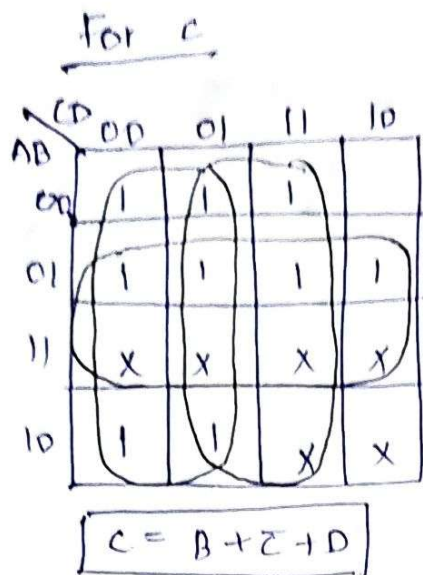

Logic diagram:

