

BECE102L-DIGITAL SYSTEMS DESIGN

Module-4

Design of data path circuits

by

Dr. Rajkishor Kumar (Ph.D. | IIT, Dhanbad)

Assistant Professor Senior Grade, School of Electronics Engineering

Vellore Institute of Technology, Vellore, Tamil Nadu, India

Email Id/ Institute ID: rajkishorkumar88@gmail.com/ rajkishor.kumar@vit.ac.in

Personal Website: <https://sites.google.com/site/rajkishormicrowave>

.....


.....

Module: 4 Design of data path circuits



Module:4 Design of data path circuits 6 hours

N-bit Parallel Adder/Subtractor, Carry Look Ahead Adder, Unsigned Array Multiplier, Booth Multiplier, 4-Bit Magnitude comparator.
Modeling of data path circuits using Verilog HDL

N-bit Parallel Adder/Subtractor

 

N Bit Adder and Subtractor

  

n -bit Parallel Subtractor Circuit Realized Using n full Adders

N bit Adder code

```
module N_bit_adder(input1,input2,answer);
  parameter N=32;
    input [N-1:0] input1,input2;
    output [N-1:0] answer;
    wire carry_out;
    wire [N-1:0] carry;
  genvar i;
  generate
    for(i=0;i<N;i=i+1)
      begin: generate_N_bit_Adder
        if(i==0)
          half_adder f(input1[0],input2[0],answer[0],carry[0]);
        else
          full_adder f(input1[i],input2[i],carry[i-1],answer[i],carry[i]);
        end
        assign carry_out = carry[N-1];
      endgenerate
endmodule
```

```
module half_adder(x,y,s,c);  
  input x,y;  
  output s,c;  
  assign s=x^y;  
  assign c=x&y;  
endmodule // half adder
```

```
module full_adder(x,y,c_in,s,c_out);  
  input x,y,c_in;  
  output s,c_out;  
  assign s = (x^y) ^ c_in;  
  assign c_out = (y&c_in) | (x&y) | (x&c_in);  
endmodule // full_adder
```

Sample testbench

```
module tb_N_bit_adder;
// Inputs
reg [31:0] input1;
reg [31:0] input2;
// Outputs
wire [31:0] answer;

// Instantiate the Unit Under Test (UUT)
N_bit_adder uut (
    .input1(input1),
    .input2(input2),
    .answer(answer)
);

initial begin
// Initialize Inputs
input1 = 1209;
input2 = 4565;
#100;
// Add stimulus here
end

endmodule
```

Verilog for full adder

```
module fulladd(a,b,carryin,sum,carryout);  
    input a, b, carryin; /* add these bits*/  
    output sum, carryout; /* results */  
  
    assign {carryout, sum} = a + b + carryin;  
        /* compute the sum and carry */  
endmodule
```


Verilog for ripple-carry adder

```
module nbitfulladd(a,b,carryin,sum,carryout)
  input [7:0] a, b; /* add these bits */
  input carryin; /* carry in*/
  output [7:0] sum; /* result */
  output carryout;
  wire [7:1] carry; /* transfers the carry between bits */

  fulladd a0(a[0],b[0],carryin,sum[0],carry[1]);
  fulladd a1(a[1],b[1],carry[1],sum[1],carry[2]);
  ...
  fulladd a7(a[7],b[7],carry[7],sum[7],carryout);
endmodule
```

Ref the code :

[Ripple carry adder code reference from textbook](#)


Carry-lookahead adder

- First compute carry propagate, generate:
 - $P_i = a_i + b_i$
 - $G_i = a_i b_i$
- Compute sum and carry from P and G:
 - $s_i = c_i \text{ XOR } P_i \text{ XOR } G_i$
 - $c_{i+1} = G_i + P_i c_i$


Carry-lookahead expansion

- Can recursively expand carry formula:
 - $c_{i+1} = G_i + P_i(G_{i-1} + P_{i-1}c_{i-1})$
 - $c_{i+1} = G_i + P_iG_{i-1} + P_iP_{i-1}(G_{i-2} + P_{i-1}c_{i-2})$
- Expanded formula does not depend on intermediate carries.
- Allows carry for each bit to be computed independently.


Depth-4 carry-lookahead

 

Carry Look Ahead Adder

 

CLA

 

Generate and Propagate

$$G[i] = A[i].B[i]$$

$$P[i] = A[i] \oplus B[i]$$

$$C[i] = G[i] + P[i].C[i-1]$$

$$S[i] = P[i] \oplus C[i-1]$$

$$G[i] = A[i].B[i]$$

$$P[i] = A[i] + B[i]$$

$$C[i] = G[i] + P[i].C[i-1]$$

$$S[i] = A[i] \oplus B[i] \oplus C[i-1]$$

Two methods to develop C[i] and S[i].

Verilog for carry-lookahead carry block

```
module carry_block(a,b,carryin,carry);
```

```
    input [3:0] a, b; /* add these bits*/
```

```
    input carryin; /* carry into the block */
```

```
    output [3:0] carry; /* carries for each bit in the block */
```

```
    wire [3:0] g, p; /* generate and propagate */
```

```
    assign g[0] = a[0] & b[0]; /* generate 0 */
```

```
    assign p[0] = a[0] ^ b[0]; /* propagate 0 */
```

```
    assign g[1] = a[1] & b[1]; /* generate 1 */
```

```
    assign p[1] = a[1] ^ b[1]; /* propagate 1 */
```

...

```
    assign carry[0] = g[0] | (p[0] & carryin);
```

```
    assign carry[1] = g[1] | p[1] & (g[0] | (p[0] & carryin));
```

```
    assign carry[2] = g[2] | p[2] & (g[1] | p[1] & (g[0] | (p[0] & carryin)));
```

```
    assign carry[3] = g[3] | p[3] & (g[2] | p[2] & (g[1] | p[1] & (g[0] | (p[0] & carryin))));
```

- endmodule

$$C_{i+1} = G_i + P_i(G_{i-1} + P_{i-1}C_{i-1})$$





Verilog for carry-lookahead adder

- ```
module carry_lookahead_adder(a,b,carryin,sum,carryout);
 input [15:0] a, b; /* add these together */
 input carryin;
 output [15:0] sum; /* result */
 output carryout;
 wire [16:1] carry; /* intermediate carries */



 assign carryout = carry[16]; /* for simplicity */
 /* build the carry-lookahead units */
 carry_block b0(a[3:0],b[3:0],carryin,carry[4:1]);
 carry_block b1(a[7:4],b[7:4],carry[4],carry[8:5]);
 carry_block b2(a[11:8],b[11:8],carry[8],carry[12:9]);
 carry_block b3(a[15:12],b[15:12],carry[12],carry[16:13]);

 sum a0(a[0],b[0],carryin,sum[0]);
 sum a1(a[1],b[1],carry[1],sum[1]);
 ...
 sum a15(a[15],b[15],carry[15],sum[15]);
endmodule
```

# Unsigned 2x2 Array Multiplier

    


# 3 x 2 / 2 x 3 Multiplier circuit

  
 
# 3 X 3 Multiplier

[www.electricaltechnology.org](http://www.electricaltechnology.org)



3-bit by 3-bit

|   | a <sub>2</sub>                | a <sub>1</sub>                | a <sub>0</sub>                |
|---|-------------------------------|-------------------------------|-------------------------------|
| x | b <sub>2</sub>                | b <sub>1</sub>                | b <sub>0</sub>                |
|   | a <sub>2</sub> b <sub>0</sub> | a <sub>1</sub> b <sub>0</sub> | a <sub>0</sub> b <sub>0</sub> |
|   | a <sub>2</sub> b <sub>1</sub> | a <sub>1</sub> b <sub>1</sub> | a <sub>0</sub> b <sub>1</sub> |
|   | a <sub>2</sub> b <sub>2</sub> | a <sub>1</sub> b <sub>2</sub> | a <sub>0</sub> b <sub>2</sub> |

|    | A2        | A1        | A0        |
|----|-----------|-----------|-----------|
| B2 | B1        | B0        |           |
|    | A2B0      | A1B0      | A0B0      |
|    | A2B1      | A1B1      | A0B1      |
|    | A2B2      | A1B2      | A0B2      |
|    | A2B2+C+C  | A2B1+A1B2 | A1B1+C+   |
|    | +A2B2+C+C | A0B2+A2B0 | A0B1+A1B0 |
|    |           |           | A0B0      |

# 4 x 3 Multiplier

 
 



Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

# Unsigned 4x4 Array Multiplier

$$\begin{array}{r}
 \begin{array}{cccc}
 a_3 & a_2 & a_1 & a_0 \\
 \times & b_3 & b_2 & b_1 & b_0 \\
 \hline
 p_{30} & p_{20} & p_{10} & p_{00} \\
 p_{31} & p_{21} & p_{11} & p_{01} & \times \\
 p_{32} & p_{22} & p_{12} & p_{02} & \times & \times \\
 p_{33} & p_{23} & p_{13} & p_{03} & \times & \times & \times \\
 \hline
 s_7 & s_6 & s_5 & s_4 & s_3 & s_2 & s_1 & s_0
 \end{array}
 \end{array}$$


Multiplication of two 4-bit unsigned numbers

|               |   |                   |
|---------------|---|-------------------|
| 1 0 1 0       | → | Multiplicand      |
| × 1 0 1 1     | → | Multiplier        |
| 1 0 1 0       | → | Partial product 1 |
| 1 0 1 0       | → | Partial product 2 |
| 0 0 0 0       | → | Partial product 3 |
| 1 0 1 0       | → | Partial product 4 |
| 1 1 0 1 1 1 0 |   |                   |

 


Unsigned Array Multiplier

# 4 x 4 Multiplier

 




# Booth Multiplier

 

Flow Chart Of Booth Multiplier Algorithm

 1. Set the Multiplicand and Multiplier binary bits as M and Q, respectively.
2. Initially, we set the AC and  $Q_{n+1}$  registers value to 0.
3. SC represents the number of Multiplier bits (Q), and it is a sequence counter that is continuously decremented till equal to the number of bits (n) or reached to 0.
4. A  $Q_n$  represents the last bit of the Q, and the  $Q_{n+1}$  shows the incremented bit of  $Q_n$  by 1.
5. On each cycle of the booth algorithm,  $Q_n$  and  $Q_{n+1}$  bits will be checked on the following parameters as follows:
  - i. When two bits  $Q_n$  and  $Q_{n+1}$  are 00 or 11, we simply perform the arithmetic shift right operation (ashr) to the partial product AC. And the bits of  $Q_n$  and  $Q_{n+1}$  is incremented by 1 bit.
  - ii. If the bits of  $Q_n$  and  $Q_{n+1}$  is shows to 01, the multiplicand bits (M) will be added to the AC (Accumulator register). After that, we perform the right shift operation to the AC and QR bits by 1.
  - iii. If the bits of  $Q_n$  and  $Q_{n+1}$  is shows to 10, the multiplicand bits (M) will be subtracted from the AC (Accumulator register). After that, we perform the right shift operation to the AC and QR bits by 1.
6. The operation continuously works till we reached  $n - 1$  bit in the booth algorithm.
7. Results of the Multiplication binary bits will be stored in the AC and QR registers.



1. Initialize the multiplicand (A), multiplier (B), accumulator (AC), and shift counter (SC).
2. Set the flag (Qn) to 0.
3. Right-shift the multiplier and Qn by one bit.
4. Examine the two least significant bits of the multiplier and Qn (bits 1 and 0). Depending on their values, perform one of three actions:
  - a. If the bits are 01, subtract the multiplicand from the accumulator.
  - b. If the bits are 10, add the multiplicand to the accumulator.
  - c. If the bits are 00 or 11, take no action.
5. Right-shift the accumulator by one bit.
6. Decrease the shift counter.
7. Repeat steps 3-6 until the shift counter reaches zero.
8. The final product is obtained by concatenating the accumulator and the shifted multiplier ([AC, B]).

Multiplicand = 7 (M) = 0111

Multiplier = 3 (Q) = 0011

Accumulator = 0(A) = 0000

| Accumulator<br>(A) | Multiplier(Q) | Test<br>Bit(T) | Operation                       | Operation<br>Number |
|--------------------|---------------|----------------|---------------------------------|---------------------|
| 0000               | 0011          | 0              | Subtraction ( $A \leq A+M'+1$ ) | I                   |
| 1001               | 0011          | 0              | Shift Right                     |                     |
| 1100               | 1001          | 1              | Shift Right                     | II                  |
| 1110               | 0100          | 1              | Addition ( $A \leq A+M$ )       | III                 |
| 0101               | 0100          | 1              | Shift Right                     |                     |
| 0010               | 1010          | 0              | Shift Right                     | IV                  |
| 0001               | 0101          | 0              | Finish                          |                     |

```

1 module Booth_Multiplier(PRODUCT, A, B);
2 output reg signed [7:0] PRODUCT;
3 input signed [3:0] A, B;
4
5 reg [1:0] temp;
6 integer i;
7 reg e;
8 reg [3:0] B1;
9
10 always @(A,B)
11 begin
12 PRODUCT = 8'd0;
13 e = 1'b0;
14 B1 = -B;
15
16 for (i=0; i<4; i=i+1)
17 begin
18 temp = { A[i], e };
19 case(temp)
20 2'd2 : PRODUCT[7:4] = PRODUCT[7:4] + B1;
21 2'd1 : PRODUCT[7:4] = PRODUCT[7:4] + B;
22 endcase
23 PRODUCT = PRODUCT >> 1;
24 PRODUCT[7] = PRODUCT[6];
25 e=A[i];

```

```
26
27 end
28 end
29
30 endmodule
31
```

## Testbench for Booth Multiplier

```
34 module tb_Booth_Multiplier;
35 wire [7:0] Y;
36 reg [3:0] A, B;
37
38 Booth_Multiplier dut(Y, A, B);
39
40 initial
41 begin
42
43 $display("RSLT\tA x B = Y"); //Results comes in signed fixed number
44 A = 2; B = 2; #10; //but if it comes in unsigned number so
45 if (Y == 4) //the answer is also correst but in that
46 $display("PASS\t%p x %p = %p",A,B,Y); //case transcript shows fail.
47 else
48 $display("FAIL\t%p x %p = %p",A,B,Y);
49
50
51 A = 3; B = 4; #10;
52 if (Y == 12)
53 $display("PASS\t%p x %p = %p",A,B,Y);
54 else
55 $display("FAIL\t%p x %p = %p",A,B,Y);
56 end
```

```
57 A = 3; B = -4; #10;
58 if (Y == -12)
59 $display("PASS\t%p x %p = %p",A,B,Y);
60 else
61 $display("FAIL\t%p x %p = %p",A,B,Y);
62
63
64 A = 0; B = 0; #10;
65 if (Y == 0)
66 $display("PASS\t%p x %p = %p",A,B,Y);
67 else
68 $display("FAIL\t%p x %p = %p",A,B,Y);
69
70
71 A = 15; B = 15; #10;
72 if (Y == 225)
73 $display("PASS\t%p x %p = %p",A,B,Y);
74 else
75 $display("FAIL\t%p x %p = %p",A,B,Y);
76
77 end
78
79 endmodule
```





## Transcript


```
Reading C:/altera/13.0spl/modelsim_ase/tcl/vsim/pref.tcl
Loading project MUX
Compile of BoothMultiplier.v was successful.
ModelSim> vsim -gui work.tb_Booth_Multiplier
vsim -gui work.tb_Booth_Multiplier
Loading work.tb_Booth_Multiplier
Loading work.Booth_Multiplier
VSIM 2> run
RSLT A x B = Y
PASS 2 x 2 = 4
PASS 3 x 4 = 12
FAIL 3 x 12 = 244
PASS 0 x 0 = 0
FAIL 15 x 15 = 1

VSIM 3>]
```

# Shift operation
 
## 1. RSC (Right Shift Circular)

It shifts the right-most bit of the binary number, and then it is added to the beginning of the binary bits.



## 2. RSA (Right Shift Arithmetic)

It adds the two binary bits and then shift the result to the right by 1-bit position.

**Example:**  $0100 + 0110 \Rightarrow 1010$ , after adding the binary number shift each bit by 1 to the right and put the first bit of resultant to the beginning of the new bit.

Example: Multiply the two numbers 7 and 3 by using the Booth's multiplication algorithm.

**Ans.** Here we have two numbers, 7 and 3.

First of all, we need to convert 7 and 3 into binary numbers like  $7 = (0111)$  and  $3 = (0011)$ .

Now set 7 (in binary 0111) as multiplicand (M) and 3 (in binary 0011) as a multiplier (Q). And SC (Sequence Count) represents the number of bits, and here we have 4 bits, so set the  $SC = 4$ .

Also, it shows the number of iteration cycles of the booth's algorithms and then cycles run  $SC = SC - 1$  time.

| $Q_n$    | $Q_{n+1}$ | $M = (0111)$<br>$M' + 1 = (1001)$ & Operation    | AC          | Q           | $Q_{n+1}$ | SC |
|----------|-----------|--------------------------------------------------|-------------|-------------|-----------|----|
| 1        | 0         | Initial                                          | 0000        | 0011        | 0         | 4  |
|          |           | <b>Subtract</b> ( $M' + 1$ )                     | 1001        |             |           |    |
|          |           |                                                  | 1001        |             |           |    |
|          |           | Perform Arithmetic Right Shift operations (ashr) | 1100        | 1001        | 1         | 3  |
| 1        | 1         | Perform Arithmetic Right Shift operations (ashr) | 1110        | 0100        | 1         | 2  |
| <b>0</b> | <b>1</b>  | Addition ( $A + M$ )                             | 0111        |             |           |    |
|          |           |                                                  | 0101        | 0100        |           |    |
|          |           | Perform Arithmetic right shift operation         | 0010        | 1010        | 0         | 1  |
| 0        | 0         | Perform Arithmetic right shift operation         | <b>0001</b> | <b>0101</b> | 0         | 0  |

- The numerical example of the Booth's Multiplication Algorithm is  $7 \times 3 = 21$  and the binary representation of 21 is 10101.
- Here, we get the resultant in binary 00010101. Now we convert it into decimal, as  $(000010101)_{10} = 2 \cdot 4 + 2 \cdot 3 + 2 \cdot 2 + 2 \cdot 1 + 2 \cdot 0 \Rightarrow 21$

```

module boothmul(input [7:0]a,b, output [15:0] c);
 wire [7:0]Q0,Q1,Q2,Q3,Q4,Q5,Q6,Q7; wire [7:0] A1,A0,A3,A2;
 wire [7:0] A4,A5,A6,A7; wire [7:0] q0; wire qout;
 booth_substep step1(8'b00000000,a,1'b0,b,A1,Q1,q0[1]);
 booth_substep step2(A1,Q1,q0[1],b,A2,Q2,q0[2]);
 booth_substep step3(A2,Q2,q0[2],b,A3,Q3,q0[3]);
 booth_substep step4(A3,Q3,q0[3],b,A4,Q4,q0[4]);
 booth_substep step5(A4,Q4,q0[4],b,A5,Q5,q0[5]);
 booth_substep step6(A5,Q5,q0[5],b,A6,Q6,q0[6]);
 booth_substep step7(A6,Q6,q0[6],b,A7,Q7,q0[7]);
 booth_substep step8(A7,Q7,q0[7],b,c[15:8],c[7:0],qout);
endmodule

module booth_substep(input [7:0]A,Q, input q0, input [7:0]M, output
[7:0]A_,Q_, output Q_1);
 wire [7:0] sum, difference;
 assign {A_,Q_,Q_1} = ((Q[0] < q0) ? {sum[7],sum,Q} : ((Q[0] > q0) ?
 {difference[7], difference, Q} : {A[7],A,Q})) ;
 ALU sub(A,~M,1'b1,difference); ALU add(A,M,1'b0,sum);
endmodule

module ALU(b,a,cin,sum);
 input [7:0] a,b; input cin; output [7:0]sum;
 assign sum = a + b + cin;
endmodule

```

```

module multiplier(prod, busy, mc, mp, clk, start);
output [15:0] prod;output busy;input [7:0] mc, mp;input clk, start;
reg [7:0] A, Q, M;reg Q_1;reg [3:0] count; wire [7:0] sum, difference;

```

```

always @(posedge clk)

```

```

begin

```

```

if (start) begin

```

```

 A <= 8'b0;M <= mc;Q <= mp;Q_1 <= 1'b0;count <= 4'b0;

```

```

endelse begin

```

```

 case ({Q[0], Q_1})

```

```

 2'b0_1 : {A, Q, Q_1} <= {sum[7], sum, Q};

```

```

 2'b1_0 : {A, Q, Q_1} <= {difference[7], difference, Q};

```

```

 default: {A, Q, Q_1} <= {A[7], A, Q}; endcase

```

```

 count <= count + 1'b1; end end

```

```

 alu adder (sum, A, M, 1'b0); alu subtracter (difference, A, ~M, 1'b1);

```

```

 assign prod = {A, Q}; assign busy = (count < 8);

```

```

endmodule

```

//The following is an alu.//It is an adder, but capable of subtraction:// subtraction means adding the two's complement--// $a - b = a + (-b) = a + (\text{inverted } b + 1)$ //The 1 will be coming in as cin (carry-in)

```

module alu(out, a, b, cin);

```

```

 output [7:0] out; input [7:0] a;input [7:0] b;input cin;

```

```

 assign out = a + b + cin;

```

```

endmodule


```

# Testbench for Booth's Multiplier

```
module testbench;
 reg clk, start; reg [7:0] a, b;
 wire [15:0] ab;
 wire busy;
 multiplier multiplier1 (ab, busy, a, b, clk, start);
 initial begin clk = 0;
 $display("first example: a = 3 b = 17"); a = 3; b = 17; start = 1; #50 start = 0; #80
 $display("first example done");
 $display("second example: a = 7 b = 7"); a = 7; b = 7; start = 1; #50 start = 0; #80
 $display("second example done");
 $finish;
 end
 always #5 clk = !clk;
 always @(posedge clk)
 $strobe("ab: %d busy: %d at time=%t", ab, busy, $stime);
endmodule
```

# 1 bit Comparator

| Inputs |   | Outputs |         |         |
|--------|---|---------|---------|---------|
| B      | A | $A > B$ | $A = B$ | $A < B$ |
| 0      | 0 | 0       | 1       | 0       |
| 0      | 1 | 1       | 0       | 0       |
| 1      | 0 | 0       | 0       | 1       |
| 1      | 1 | 0       | 1       | 0       |

 



# 2 bit Comparator

| INPUT |    |    |    | OUTPUT |     |     |
|-------|----|----|----|--------|-----|-----|
| A1    | A0 | B1 | B0 | A<B    | A=B | A>B |
| 0     | 0  | 0  | 0  | 0      | 1   | 0   |
| 0     | 0  | 0  | 1  | 1      | 0   | 0   |
| 0     | 0  | 1  | 0  | 1      | 0   | 0   |
| 0     | 0  | 1  | 1  | 1      | 0   | 0   |
| 0     | 1  | 0  | 0  | 0      | 0   | 1   |
| 0     | 1  | 0  | 1  | 0      | 1   | 0   |
| 0     | 1  | 1  | 0  | 1      | 0   | 0   |
| 0     | 1  | 1  | 1  | 1      | 0   | 0   |
| 1     | 0  | 0  | 0  | 0      | 0   | 1   |
| 1     | 0  | 0  | 1  | 0      | 0   | 1   |
| 1     | 0  | 1  | 0  | 0      | 1   | 0   |
| 1     | 0  | 1  | 1  | 1      | 0   | 0   |
| 1     | 1  | 0  | 0  | 0      | 0   | 1   |
| 1     | 1  | 0  | 1  | 0      | 0   | 1   |
| 1     | 1  | 1  | 0  | 0      | 0   | 1   |
| 1     | 1  | 1  | 1  | 0      | 1   | 0   |

$$A > B: A1B1' + A0B1'B0' + A1A0B0'$$




$$A = B: A1'A0'B1'B0' + A1'A0B1'B0 + A1A0B1B0 + A1A0'B1B0' : A1'B1' (A0'B0' + A0B0) + A1B1 (A0B0 + A0'B0') : (A0B0 + A0'B0') (A1B1 + A1'B1') : (A0 \odot B0) (A1 \odot B1)$$

$$A < B: A1'B1 + A0'B1B0 + A1'A0'B0$$

$$A=B$$

- The condition of  $A=B$  is possible only when all the individual bits of one number exactly coincide with corresponding bits of another number.
- $A=B: A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0 + A_1A_0'B_1B_0'$   
 $: A_1'B_1' (A_0'B_0' + A_0B_0) + A_1B_1 (A_0B_0 + A_0'B_0')$   
 $: (A_0B_0 + A_0'B_0') (A_1B_1 + A_1'B_1')$   
 $A=B: (A_0 \odot B_0) (A_1 \odot B_1)$

# 4-Bit Magnitude comparator

   

$$A > B$$

- In a 4-bit comparator the condition of  $A > B$  can be possible in the following four cases:
- If  $A_3 = 1$  and  $B_3 = 0$
- If  $A_3 = B_3$  and  $A_2 = 1$  and  $B_2 = 0$
- If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 1$  and  $B_1 = 0$
- If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 1$  and  $B_0 = 0$


$$A < B$$

- Similarly the condition for  $A < B$  can be possible in the following four cases:
- If  $A_3 = 0$  and  $B_3 = 1$
- If  $A_3 = B_3$  and  $A_2 = 0$  and  $B_2 = 1$
- If  $A_3 = B_3$ ,  $A_2 = B_2$  and  $A_1 = 0$  and  $B_1 = 1$
- If  $A_3 = B_3$ ,  $A_2 = B_2$ ,  $A_1 = B_1$  and  $A_0 = 0$  and  $B_0 = 1$

# 1 bit Comparator verilog code



```
module comp_1bit(a,b,lt,eq,gt);
 input a,b;
 output lt,gt,eq;
 wire abar,bbar;
 assign abar = ~a;
 assign bbar = ~b;
 assign lt = abar & b;
 assign gt = bbar & a;
 assign eq = ~(lt|gt);
endmodule
```

# 1 bit comparator using 4:1 MUX

 
  
# 1 bit comparator

<https://circuitverse.org/simulator/edit/comparator-1b4f8e41-fc1f-4d7a-8028-fb7803da64f3>



<https://circuitverse.org/simulator/edit/1-bit-comparator-61c9165d-1870-4a14-8bb8-8cfa3cebc8e4>



## N bit and 4 bit comparator circuits

 
 
 


Fig 2: 4-Bit Comparator using 1-bit Cascaded Comparator

# 4 bit comparator Verilog code

```
module comparator4(A,B,LT1,GT1,EQ1,LT2,GT2,EQ2);
 input [3:0] A,B;
 output LT2,GT2,EQ2;
 input LT1,GT1,EQ1;
 wire x30,x31,x32,x20,x21,x22,x10,x11,x12,x00,x01,x02;
 wire x40,x41,x42,x50,x51,x52,x61,x62;
 comp_1bit c3(A[3],B[3],x30,x31,x32);
 comp_1bit c2(A[2],B[2],x20,x21,x22);
 comp_1bit c1(A[1],B[1],x10,x11,x12);
 comp_1bit c0(A[0],B[0],x00,x01,x02);
```

```
assign x40 = x31 & x20;
 assign x41 = x31 & x21 & x10;
 assign x42 = x31 & x21 & x11 & x00;
 assign x50 = x31 & x22;
 assign x51 = x31 & x21 & x12;
 assign x52 = x31 & x21 & x11
& x02;

 assign EQ = (x31 & x21 & x11 & x01);
 assign EQ2 = EQ & EQ1;
 assign x61 = EQ & LT1;
 assign x62 = EQ & GT1;
 assign LT2 = (x30 | x40 | x41 | x42) | x61;
 assign GT2 = (x32 | x50 | x51 | x52) | x62;

endmodule
```

# The Verilog code for the 16-bit Comparator

```
module comp16(a,b,lt1,gt1,eq1);
 input [15:0] a,b; output lt1,gt1,eq1;
 parameter eq =1'b1; parameter lt=1'b0;
 parameter gt=1'b0;
 wire t11,t12,t13,t21,t22,t23,t31,t32,t33;

 comparator4 c1(a[3:0],b[3:0],lt,gt,eq,t11,t12,t13);
 comparator4 c2(a[7:4],b[7:4],t11,t12,t13,t21,t22,t23);
 comparator4 c3(a[11:8],b[11:8],t21,t22,t23,t31,t32,t33);
 comparator4 c4(a[15:12],b[15:12],t31,t32,t33,lt1,gt1,eq1);
endmodule
```

# REFERENCE

- <https://technobyte.org/2-bit-4-bit-comparator/>  
VERILOG CODES FOR CLC:
- <https://digitalsystemdesign.in/wp-content/uploads/2018/05/Combinational-Curcuits.pdf>