 




Digital Systems Design : BECE102L

Blocking and Non-Blocking Assignment in Behavioural Modelling



Dr. Vetriveeran Rajamani,
Associate Professor Grade 1,
Department of Micro and Nano Electronics,
School of Electronics Engineering (SENSE),
VIT Vellore.

The assignment statements so far

	Continuous Assignment	Procedural Assignment
Operation	=	=
Where	using stand-alone <i>assign</i> statement	inside of <i>always</i> and <i>initial</i>
Example	<pre>wire q; reg a, b; assign q = a & b;</pre>	<pre>wire q; reg a, b; always @(b) a = b + 5;</pre>
Valid LHS	net (wire)	reg
Valid RHS	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution

What is 'procedural execution' ?

- ❑ An always block is either executing, or it is waiting for an event from its sensitivity list
- ❑ When it is executing, it proceeds in a sequential fashion through the statements of the code, until it runs into an *event control statement* (@, wait, #)

```
always begin
```


```
@(upedge a) ;
```

```
b = a + 1 ;
```

```
wait (c == 3) ;
```


```
#20 b = a + 1 ;
```

```
end
```

 

What is 'procedural execution' ?

 - ❑ An always is either executing, or it is waiting for an event from its *sensitivity list*
- ❑ When it is executing, it proceeds in a sequential fashion through the statements of the code, until it runs into an *event control statement* (@, wait, #)



The assignment statements so far

	Continuous Assignment	Procedural Assignment
Operation	=	=
Where used	continuous assignment	always
Example		The full name of this assignment is: Procedural <i>Blocking</i> Assignment <pre>a = b + 5;</pre>
Valid LHS	net (wire)	reg
Valid RHS	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    a = b + 2;  
    b = a * 3;  
end
```

Blocking assignment:

assignment on *a* MUST complete before
assignment on *b* can start

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #10 a = b + 2;  
    b = a * 3;  
end
```

1. **Wait 10;**
2. Read value of b and add 2 to it;
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    a = #10 b + 2;  
    b = a * 3;  
end
```

1. Read value of b and add 2 to it;
2. **Wait 10;**
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #5 a = #10 b + 2;  
    #5 b = a * 3;  
end
```

1. **Wait 5;**
2. Read value of b and add 2 to it;
3. **Wait 10;**
4. Assign the result to a;
5. **Wait 5;**
6. Read the value of a and multiply by three;
7. Assign the result to b;

Procedural Blocking Assignment

- ❑ Execution in a sequential block cannot complete without the assignment being complete

*Blocking Assignment means
a will always be assigned before b*

```
reg [7:0] a, b;  
always @(posedge clk) begin  
    #5 a = #10 b + 2;  
    #5 b = a * 3;  
end
```

1. **Wait 5;**
2. Read value of b and add 2 to it;
3. **Wait 10;**
4. **Assign the result to a;**
5. **Wait 5;**
6. Read the value of a and multiply by three;
7. **Assign the result to b;**

Procedural Non-Blocking Assignment

	Continuous Assignment	Proc. Blocking Assignment	Proc. Non-Blocking Assignment
Operation	=	=	<=
Where	using stand-alone <i>assign</i> statement	inside of <i>always</i> and <i>initial</i>	inside of <i>always</i> and <i>initial</i>
Example	<pre>wire q; reg a, b; assign q = a & b;</pre>	<pre>wire q; reg a, b; always @(b) a = b + 5;</pre>	<pre>wire q; reg a, b; always @(b) a <= 5;</pre>
Valid LHS	net (wire)	reg	reg
Valid RHS	expression of net or reg	expression of net or reg	expression of net or reg
Evaluated	when any part of RHS changes	procedural execution	at the end of current time step

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;  
  
initial b = 0;  
initial a = 4;  
  
always @(a or b)  
begin  
    a = b + 2;  
    b = a * 3;  
end
```

Non-Blocking

```
reg [7:0] a, b;  
  
initial b = 0;  
initial a = 4;  
  
always @(a or b)  
begin  
    a <= b + 2;  
    b <= a * 3;  
end
```

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a = b + 2;
```

```
    b = a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 2 * 3 = 6$

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a <= b + 2;
```

```
    b <= a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 4 * 3 = 12$

Effect of a non-blocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
ini
```

```
always @(a or b)
```

```
begin
```

```
    a = b + 2;
```

```
    b = a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 2 * 3 = 6$

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
ini
```

```
always @(a or b)
```

```
begin
```

```
    a <= b + 2;
```

```
    b <= a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 4 * 3 = 12$

*Non-Blocking Assignment means
a and b are updated at the same time*

Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input  clk, in;  
    reg    q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```



Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input  clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

Another example

Using blocking assignments:


```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input  clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

Another example


Using non-blocking assignments:

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
endmodule
```

 


Think about the *meaning* of this behavior

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 = in;  
        q0 = in | q1;  
    end  
endmodule
```

 

```
module fsm_mod(q1, q0, in, clk);  
    output q1, q0;  
    input clk, in;  
    reg q1, q0;  
  
    always @(posedge clk) begin  
        q1 <= in;  
        q0 <= in | q1;  
    end  
endmodule
```

 

I. Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within always blocks, with subtly different behaviors.
- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
x = a | b;
```

1. Evaluate $a | b$, assign result to x

```
y = a ^ b ^ c;
```

2. Evaluate $a^b c$, assign result to y

```
z = b & ~c;
```

3. Evaluate $b \& (\sim c)$, assign result to z

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
x <= a | b;
```

1. Evaluate $a | b$ but defer assignment of x

```
y <= a ^ b ^ c;
```

2. Evaluate $a^b c$ but defer assignment of y

```
z <= b & ~c;
```

3. Evaluate $b \& (\sim c)$ but defer assignment of z



```
end
```

4. Assign x , y , and z with their new values

- Sometimes, as above, both produce the same result. Sometimes, not!


Why two ways of assigning values?

Conceptual need for **two kinds of assignment** (in `always` blocks):

  		
Blocking: Evaluation and assignment are immediate	$a = b$ $b = a$	$x = a \& b$ $y = x c$
Non-Blocking: Assignment is postponed until all r.h.s. evaluations are done	$a <= b$ $b <= a$	$x <= a \& b$ $y <= x c$
When to use: (only in <code>always</code> blocks!)	Sequential Circuits	Combinational Circuits

Assignment Styles for Sequential Logic

*Flip-Flop Based
Digital Delay
Line*

 

- Will nonblocking and blocking assignments both produce the desired result?


```
module nonblocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```

Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
  q1 <= in;
  q2 <= q1;
  out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out **simultaneously receive the old values** of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
  q1 = in;
  q2 = q1;
  out = q2;
end
```

 “At each rising clock edge, $q1 = in$.
After that, $q2 = q1 = in$; After that,
 $out = q2 = q1 = in$; Finally $out = in$.”



- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

Summary of Blocking and Non-Blocking Assignments

Feature	Blocking Assignment (=)	Non-Blocking Assignment (<=)
Execution	Sequential	Parallel
Use Case	Combinational logic (within always @(*) blocks)	Sequential logic (within always @(posedge clk) or negedge clk blocks)
Purpose	Modeling behavioral flow, like a software program.	Modeling hardware registers and flip-flops.
Synthesizability	Can lead to non-synthesizable code if used for sequential logic.	Ensures predictable and synthesizable sequential logic.