


Digital Systems Design (BECE102L)

Dr Vishal Gupta

Assistant Professor

School of Electronics Engineering

 Vellore Institute of Technology,
Vellore, Tamil Nadu, India



Module – 2

Verilog HDL

(Behavioral Modeling)



Behavioral Modeling in Verilog

- Specifies **how a particular design should respond to a given set of input.**
- Behavioral modelling uses **structured procedures** to specify the behaviour of the circuit.
- May be specified by **Boolean expressions.**
- **Algorithms written in standard HLL like C**

Ex : {Carry,Sum} = a+b+c;

Key Concepts

- ✓ **Continuous Assignment:** Use assign statements for combinational logic.
- ✓ **Procedural Blocks:** Use always or initial blocks to describe behavior.
- ✓ **Sensitivity List:** Defines when the always block should be triggered.
- ✓ **Blocking vs. Non-blocking Assignments:** Use = for blocking and <= for non-blocking assignments.

Behavioral Modeling in Verilog

- The **behavioral description** is a powerful tool to describe systems for which **digital logic structures are not known or are hard to generate**.
- Examples of such systems are **complex arithmetic units, computer control units, and biological mechanisms** that describe the physiological action of certain organs such as the kidney or heart.
- The behavioral description describes the system by showing how outputs **behave with the changes in inputs**. It focuses on the functionality and operation of the design rather than the implementation details.
- In this description, **details of the logic diagram of the system are not needed**; what is needed is **how the output behaves in response to a change in the input**.
- In Verilog, the major behavioral-description statements are **always** and **initial**.

Structured Procedures

- Two basic structured procedure statements or procedural blocks are
 - **always** (synthesizable)
 - **initial** (non-synthesizable)
- All behavioral statements can appear only inside these blocks.
- Each always or initial block has a separate activity flow (concurrency).
- There can be multiple always and initial blocks in a module.
- All procedural blocks start from simulation time 0.
- Can not be nested.

Structured Procedures: **always** statement

- Starts at time 0.
- Execute the statements in a looping fashion or **activity** that is **repeated continuously** in a digital circuit.
- Multiple always blocks, execute in parallel. All start at time 0.
- Equivalent to an **infinite loop**.
- **Stopped only** by **\$finish (close the environment)** or **\$stop (interrupt)**.

Syntax:

always @(sensitivity list)

begin

// behavioral statements

end

Structure of the HDL Behavioral Description

Verilog Description

```
module half_add (I1, I2, O1, O2);  
input I1, I2;  
output O1, O2;  
reg O1, O2;  
  
/* Since O1 and O2 are outputs, they should be declared as  
reg */  
  
always @(I1, I2)  
  
begin  
  
#10 O1 = I1 ^ I2; // statement 1.  
#10 O2 = I1 & I2; // statement 2.  
  
/*The above two statements are signal-assignment  
statements with 10 simulation screen units Delay*/  
  
/*Other behavioral (sequential) statements can be  
added here*/  
end  
endmodule
```

- Referring to the Verilog code **always** is the Verilog behavioral statement.
- All Verilog statements inside **always** are treated as **concurrent**, the same as in the **data-flow description**.
- Also, here **any signal that is declared as an output** or appears at the left-hand side of a signal-assignment statement should be **declared as a register (reg) if it appears inside always**.
- O1 and O2 are declared **outputs**, so they **should also be declared as reg**.

Behavioral Modelling – Half Adder

//Half Adder : Behavioral description

```
module ha_beh (x,y,s,c);  
input x,y;  
output s,c;  
reg s, c;  
always @(x or y)  
begin  
s = x ^ y;  
c = x & y;  
//{c,s} = x + y;  
end  
endmodule
```


Behavioral Modelling – Example

"always" block example:

```
module and_or_gate (out, in1, in2, in3);
```

```
    input    in1, in2, in3;
```

```
    output   out;
```

```
    reg      out;
```

"reg" type declaration. Not really a register in this case. Just a Verilog rule.

```
    always @(in1 or in2 or in3) begin
```

```
        out = (in1 & in2) | in3;
```

```
    end
```

"sensitivity" list, triggers the action in the body.

keyword

brackets multiple statements (not necessary in this example).

```
endmodule
```

Behavioral Modelling – 2:1 Mux

//Behavioral modelling of 2:1 Mux

```
module mux (m_out, A, B, select);  
    output m_out;  
    input A, B, select;  
    reg m_out;  
    always @(A or B or select)  
    begin  
        if (select == 1)  
            m_out = A;  
        else  
            m_out = B;  
        end  
    end  
endmodule
```

Behavioral Modelling – T Flip Flop

//Behavioral modelling of T Flip-flop

```
module t_ff(clk,rst,t,q);  
  input clk,rst,t;  
  output reg q;  
  always@(posedge clk or posedge rst)  
  begin  
    if(rst == 1)  
      q <= 0;  
    else  
      if (t == 0)  
        q <= q;  
      else  q <= ~q;  
    end  
  endmodule
```

Test Bench: T Flip Flop

//Test Bench of T Flip-flop

```
module tb();
```

```
reg clk, rst, t;
```

```
wire q;
```

```
t_ff uut(clk, rst, t, q);
```

```
always
```

```
begin
```

```
#10 clk = ~clk;
```

```
end
```

```
initial
```

```
begin
```

```
clk = 0; rst = 0; t = 0;
```

```
#5 rst = 1;
```

```
#5 rst = 0; t = 0; #15 t = 1; #10 t = 0; #15 t = 1;
```

```
#5 rst = 1;
```

```
#5 rst = 0; t = 1;
```

```
#500 $stop;
```

```
end
```

```
endmodule
```

The **initial** Statement

- An initial block –

initial begin

...

end

- It may consist of a **group of statements** (within begin ... end) or **one statement**.
- Each initial block starts at **execution time 0**.
- All **initial blocks** starts **concurrently** executing and **finishes independent** of each other.
- Typically **used for** **initialization, monitoring, waveforms** and to execute **one-time executable processes**.

Sequential Statements

- There are several statements associated with behavioral descriptions.
- These statements have to **appear inside always or initial** in Verilog.
- The following sections discuss some of these statements.

1. IF Statement:

Verilog IF-Else Formats

```
if (Boolean Expression)
begin
    statement 1; /* if only one statement, begin and end
                  can be omitted */
    statement 2;
    statement 3;
    .....
end
else
begin
    statement a; /* if only one statement, begin and end
                  can be omitted */
    statement b;
    statement c;
    .....
end
```

- **IF** is a **sequential statement** that appears inside **always** or **initial** in Verilog.
- The execution of IF statement is controlled by the Boolean expression.
- If the Boolean expression is true, then statements 1, 2, and 3 are executed.
- If the expression is false, statements a, b, and c are executed.

Contd...

Verilog

```
if (clk == 1'b1)
// 1'b1 means 1-bit binary number of value 1.
temp = s1;
else
temp = s2;
```

if clk is high (1), the value of s1 is assigned to the variable temp. Otherwise, s2 is assigned to the variable temp.

Contd...

EXECUTION OF IF AS ELSE-IF

Verilog

```
if (Boolean Expression1)
begin
    statement1; statement 2;.....
end
else if (Boolean expression2)
begin
    statementi; statementii;.....
end
else
begin
    statementa; statement b;....
end
```

J-K Flip Flop using 'If' Statement

```
module jk_flip_flop (  
    input clk,  
    input reset,  
    input j,  
    input k,  
    output reg q);  
    always @(posedge clk or posedge reset)  
    begin  
        if (reset == 1)  
            begin  
                q <= 1'b0;  
            end  
        else  
            begin  
                if (j == 1'b0 && k == 1'b0)  
                    begin  
                        q <= q;  
                    end  
                end  
            end  
        end
```

```
    else  
        if (j == 1'b0 && k == 1'b1)  
            begin  
                q <= 1'b0;  
            end  
        else  
            if (j == 1'b1 && k == 1'b0)  
                begin  
                    q <= 1'b1;  
                end  
            else  
                if (j == 1'b1 && k == 1'b1)  
                    begin  
                        q <= ~q;  
                    end  
                end  
            end  
        end  
    end  
endmodule
```

Contd...

2. The case Statement

The **case statement** is a sequential control statement.

Verilog Case Format

```
case (control-expression)
test value1 : begin statements1; end
test value2 : begin statements2; end
test value3 : begin statements3; end
default : begin default statements end
endcase
```

Verilog

```
case sel
2'b00 : temp = I1;
2'b01 : temp = I2;
2'b10 : temp = I3;
default : temp = I4;
endcase
```

J-K Flip Flop using Case Statement

```
module jk_flip_flop (  
    input clk,  
    input reset,  
    input j,  
    input k,  
    output reg q);  
always @(posedge clk or posedge  
reset)  
    begin  
        if (reset == 1)  
            begin  
                q <= 1'b0;  
            end  
        else  
            begin
```

```
                case ({j, k})  
                    2'b00: begin q <= q; end  
                    2'b01: begin q <= 1'b0; end  
                    2'b10: begin q <= 1'b1; end  
                    2'b11: begin q <= ~q; end  
                    default: begin q <= 1'bx; end  
                endcase  
            end  
        end  
    endmodule
```

Example of case statement (ALU design)

```


module alu(f,a,b,op);
  input [1:0] op; // operation [00: a+b; 01:a-b; 10: a*b; 11: a/b
  input [7:0] a,b;
  output reg [7:0] f;
  always@(*)
  begin
    case (op)
      2'b00: f<=a+b;
      2'b01: f<=a-b;
      2'b10: f<=a*b;
      2'b11: f<=a/b;
    endcase
  end
endmodule

```

```

module tb();
  reg [1:0] op;
  reg [7:0] a,b;
  wire [7:0] f;
  alu uut(f,a,b,op);
  initial
  begin
    a=8'b11; b=8'b10; op=2'b00;
    #20 op=2'b01;
    #20 op=2'b10;
    #20 op=2'b11;
    #20;
    $finish;
  end
endmodule

```

 

Contd...

The casex and casez Statements

casez:

- It does **not compare z-values** in the condition and case options.
- It ignores the z value.

casex :

- It does **not compare x** values in the condition and case options.
- It ignores the x value.

Example of casex statement

• Priority encoder circuit

```

module
casexexample(x,y,v,d);
  input [3:0]d;
  output reg x,y,v;
  always@(d)
  begin
    casex(d)
      4'b0000: {x,y,v}=3'bXX0;
      4'b0001: {x,y,v}=3'b001;
      4'b001X: {x,y,v}=3'b011;
      4'b01XX: {x,y,v}=3'b101;
      4'b1XXX: {x,y,v}=3'b111;
    endcase
  end
endmodule

```

```

//test bench
module tb();
  reg [3:0]d;
  wire x,y,v;
  casexexample uut(x,y,v,d);
  initial
    begin
      d=4'b0000;
      #10 d=4'b0001;
      #10 d=4'b0010;
      #10 d=4'b0011;
      #10 d=4'b0100;
      #10 d=4'b0111;
      #10 d=4'b1000;
      #10 d=4'b1010;
      $finish;
    end
endmodule

```

Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Contd...

3. Wait or Dealy Statement

10; // wait for 10 time instances i.e. 10 second or 10 ps etc.

Inter-statement delays: happen between statements, with a delay on the left side of an assignment

#5 c = a + b;

Intra-statement delays: occur within a single statement, evaluated at the current time, and the result is assigned after a delay on the right side

c = #5 (a + b);

Contd...

4. Loop statement

- Loop is a **sequential statement** that has to appear **inside always or initial** in Verilog.
- **Loop** is used to repeat the execution of statements written inside its body.
- The number of **repetitions** is controlled by the range of an **index** parameter.
- The **loop allows the code to be compressed**; instead of writing a block of code as individual statements, it can be written as **one general statement** that, **if repeated, reproduces all statements** in the block.

Contd...

- **for loop:**

```
for (i = 0; i <= 2; i = i + 1)
begin
if (temp[i] == 1'b1)
begin
result = result + 2**i;
end
end
statement1;
statement2; ....
```

- **while loop:**

```
while (condition)
Statement1;
Statement2;
.....
end
```

```
while (i < x)
begin
i = i + 1;
z = i * z;
end
```

- **repeat:**

- ✓ In Verilog, the sequential statement repeat causes the execution of statements between its begin and end to be repeated a fixed number of times;
- ✓ no condition is allowed in repeat.

```
repeat (32)
begin
#100 i = i + 1;
end
```

- **forever:**

- ✓ The statement forever in Verilog repeats the loop endlessly. One common use for forever is to generate clocks in code-oriented test benches.
- ✓ The following code describes a clock with a period of 20 screen time units:

```
initial
begin
Clk = 1'b0;
forever #20 clk = ~clk;
end
```

Procedural Assignment

Two types: **Blocking Assignments** and **Non-Blocking Assignments**

1. Blocking Assignments ('='):

Execute sequentially, meaning the next statement in the block won't execute until the current one is fully completed.

Ex: Given $a = 4$, $b = 2$, $c = 1$, $d = 4$, $e = 2$

// Combinational logic example (always @())*

always @() begin*

a = b + c; // b + c is calculated, then assigned to a; a = 2 + 1 = 3

d = a - e; // The new value of a is used in this calculation; d = 3 - 2 = 1

end

Procedural Assignment

- Non-Blocking Assignments ('<='):

Evaluate all their right-hand sides (RHS) first and update the left-hand sides (LHS) at the end of the time step, allowing for simultaneous updates.

Ex: Given $a = 4$, $b = 2$, $c = 1$, $d = 4$, $e = 2$

// Combinational logic example (always @())*

always @() begin*

a <= b + c; // b + c is calculated, then assigned to a; a = 2 + 1 = 3

d <= a - e; // The new value of a is used in this calculation; d = 4 - 2 = 2

end

Blocking Assignments

- It is denoted by “=” operator.
- In a sequential block it blocks any statement beyond it.

```
reg [7:0] a, b;  
always @(posedge clk)  
begin  
    a = b + 2;  
    b = a * 3;  
end
```

Blocking assignment:

assignment on *a* MUST complete before
assignment on *b* can start

Example 1

```

module
block1(c,d,a,b,clk);
    input clk;
    input [7:0] a, b;
    output reg [7:0]c,d;
    reg [7:0] temp1,temp2;


    always @(posedge clk)
    begin
        temp1 = a;
        temp2 = b;
        temp1 = temp2 + 2;
        temp2 = temp1 * 3;
        c = temp1;
        d = temp2;
    end
endmodule

module block1_tb();
    reg clk;
    reg [7:0] a, b;
    wire [7:0] c,d;
    block1 uut(c,d,a,b,clk);

    always
    #5 clk=~clk;

    initial
    begin
        clk=0; a=8'h2; b=8'h3;
        #50;
    end
endmodule

```

 

Blocking Assignments

```
reg [7:0] a, b;
```

```
always @(posedge clk)
```

```
begin
```

```
#10 a = b + 2;
```

```
b = a * 3;
```

```
end
```

1. **Wait 10;**
2. Read value of b and add 2 to it;
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

```
reg [7:0] a, b;
```

```
always @(posedge clk)
```

```
begin
```

```
a = #10 b + 2;
```

```
b = a * 3;
```

```
end
```


1. Read value of b and add 2 to it;
2. **Wait 10;**
3. Assign the result to a;
4. Read the value of a and multiply by three;
5. Assign the result to b;

Example 2

```
module
block2(c,d,a,b,clk);
  input clk;
  input [7:0] a, b;
  output reg [7:0] c,d;
  reg [7:0] temp1,temp2;
```

```
  always @(posedge clk)
  begin
    temp1=a;
    temp2=b;
    #10 temp1 = temp2 + 2;
    temp2 = temp1 * 3;
    c=temp1;
    d=temp2;
  end
endmodule
```

```
module block2_tb();
  reg clk;
  reg [7:0] a, b;
  wire [7:0] c,d;
  block2 uut(c,d,a,b,clk);
  always
  #5 clk=~clk;
  initial
  begin
    clk=0; a=8'h2; b=8'h3;
    #50;
  end
endmodule
```

 

Example 3

```

module
block3(c,d,a,b,clk);
  input clk;
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;

  always @(posedge clk)
  begin
    temp1=a;
    temp2=b;
    temp1 = #10 temp2 + 2;
    temp2 = temp1 * 3;
    c=temp1;
    d=temp2;
  end
endmodule


```

```

module block3_tb();
  reg clk;
  reg [7:0] a, b;
  wire [7:0]c,d;
  block3 uut(c,d,a,b,clk);

  always
  #5 clk=~clk;
  initial
  begin
    clk=0; a=8'h2; b=8'h3;
    #50;
  end
endmodule

```

 

Blocking Assignments

```
reg [7:0] a, b;
```

```
always @(posedge clk)
```

```
begin
```

```
#5 a = #10 b + 2;
```

```
#5 b = a * 3;
```

```
end
```

1. **Wait 5;**
2. Read value of b and add 2 to it;
3. **Wait 10;**
4. Assign the result to a;
5. **Wait 5;**
6. Read the value of a and multiply by three;
7. Assign the result to b;

Example 4

```

module block4(c,d,a,b,clk);
  input clk;
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;


  always @(posedge clk)
  begin
    temp1=a;
    temp2=b;
    #5 temp1 = #10 temp2 + 2;
    #5 temp2 = temp1 * 3;
    c=temp1;
    d=temp2;
  end
endmodule

```

```

module block4_tb();
  reg clk;
  reg [7:0] a, b;
  wire [7:0]c,d;
  block4 uut(c,d,a,b,clk);
  always
  #5 clk=~clk;
  initial
  begin
    clk=0; a=8'h2; b=8'h3;
    #50;
  end
endmodule

```

 

Nonblocking Assignments

- These assignments **do not block execution of statements** that follow them in a sequential block.
- They are denoted by “<=” operator.
- The simulator processes all the events with a given timestamp according to the nature of the event.

❑ **Given the set of evaluate-events at time T**

❑ **First, do the following (in any order)**

- ✓ Evaluate the RHS of *all* assignments
- ✓ Assign the LHS of all procedural blocking assignments
- ✓ Assign the LHS of all continuous assignments
- ✓ Evaluate inputs and outputs of all primitives (gates)
- ✓ Print \$display statements

❑ **Then, do the following (in any order)**

- ✓ Change the LHS of all nonblocking assignments

❑ **Then, do the following (in any order)**

- ✓ Print \$monitor statements

Example: Effect of nonblocking statement

Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a = b + 2;
```

```
    b = a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 2 * 3 = 6$

Non-Blocking

```
reg [7:0] a, b;
```

```
initial b = 0;
```

```
initial a = 4;
```

```
always @(a or b)
```

```
begin
```

```
    a <= b + 2;
```

```
    b <= a * 3;
```

```
end
```

$a = 0 + 2 = 2$

$b = 4 * 3 = 12$

Non-Blocking Assignment means a and b are updated at the same time

Example 4

```

module nonblock1(c,d,a,b);
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;

  always @(a or b)
  begin
    temp1<=a;
    temp2<=b;
    temp1 <= #10 temp2 + 2;
    temp2 <= #10 temp1 * 3;
    c<=temp1;
    d<=temp2;
  end
endmodule


```

```

module nonblock1_tb();
  reg [7:0] a, b;
  wire [7:0] c,d;
  nonblock1 uut(c,d,a,b);

  initial
  begin
    a=8'h2; b=8'h3;
    #50;
  end
endmodule

```

 


Example 5

```
module
nonblock1(c,d,a,b);
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;
```

```
  always @(a or b)
  begin
    temp1<=a;
    temp2<=b;
    temp1 <= #10 temp2 + 2;
    temp2 <= #10 temp1 * 3;
    c=temp1;
    d=temp2;
  end
endmodule
```

```
module nonblock1_tb();
  reg [7:0] a, b;
  wire [7:0] c,d;
  nonblock1 uut(c,d,a,b);
```

```
  initial
  begin
    a=8'h2; b=8'h3;
    #50;
  end
endmodule
```

 

Example 6

```

module nonblock1(c,d,a,b);
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;

  always @(a or b)
  begin
    temp1=a;
    temp2=b;
    temp1 <= #10 temp2 + 2;
    temp2 <= #10 temp1 * 3;
    c=temp1;
    d=temp2;
  end
endmodule


```

```

module nonblock1_tb();
  reg [7:0] a, b;
  wire [7:0] c,d;
  nonblock1 uut(c,d,a,b);

  initial
  begin
    a=8'h2; b=8'h3;
    #50;
  end
endmodule

```

 

Example 7

```


module
nonblock1(c,d,a,b);
  input [7:0] a, b;
  output reg [7:0]c,d;
  reg [7:0] temp1,temp2;

  always @(a or b)
  begin
    temp1=a;
    temp2=b;
    temp1 = #10 temp2 + 2;
    temp2 = #10 temp1 * 3;
    c<=temp1;
    d<=temp2;
  end
endmodule

module nonblock1_tb();
  reg [7:0] a, b;
  wire [7:0] c,d;
  nonblock1 uut(c,d,a,b);

  initial
  begin
    a=8'h2; b=8'h3;
    #50;
  end
endmodule

```

 


Example (blocking)

```
module fsm_mod(q1,q0,in,clk);
  input in,clk;
  output reg q1,q0;
  always @(posedge clk) begin
    q1=in;
    q0=in|q1;
  end
endmodule
```

```
module fsm_tb();
  reg in,clk;
  wire q1,q0;
  fsm_mod uut(q1,q0,in,clk);
  always
    #10 clk=~clk;

   initial begin
    clk=0; in=0;
    #45 in=1;
    #40 in=0;
    #100;
    $stop;
  end
endmodule
```




Example: (nonblocking)

```
module fsm_mod(q1,q0,in,clk);
  input in,clk;
  output reg q1,q0;
  always @(posedge clk) begin
    q1<=in;
    q0<=in|q1;
  end
endmodule
```

```
module fsm_tb();
  reg in,clk;
  wire q1,q0;
  fsm_mod uut(q1,q0,in,clk);
  always
    #10 clk=~clk;

   initial begin
    clk=0; in=0;
    #45 in=1;
    #40 in=0;
    #100;
    $stop;
  end
endmodule
```




Delays and blocking assignments

```

initial
begin
    a = 1;           t = 0: assign a with 1
    #5 b = a + 1;    t = 5: evaluate a + 1 and assign b
end
    
```

```

 module test4();
    reg [3:0] a,b;
    initial
    begin
        a=1;
        #5 b=a+1;
    end
endmodule
    
```



Delays and nonblocking assignments

```
initial
begin
    a <= 1;
    #5 b <= a + 1;
end
```

t = 0: assign a with 1 at the end of timestep 0
t = 5: evaluate a + 1 and assign b at the end of timestep 5

```
module test5();
reg [3:0] a,b;
initial
begin
    a<= 1;
    #5 b<=a+1;
end
endmodule
```




Contd...

```

initial
  a = 0;
initial
  #5 a = a + 1;      t = 5: a is assigned with 1
initial
  #5 b = a + 1;      t = 5: b is indeterminate, because a changes
                    at t=5 using a blocking assignment
  
```

```

 module test6();
  reg [3:0] a,b;
  initial
    a=0;
  initial
    #5 a=a+1;
  initial
    #5 b=a+1;
endmodule
  
```



Contd...

```
initial
```

```
    a = 0;
```

```
initial
```

```
    #5 a <= a + 1;      t = 5: a is assigned with 1 at the end of t=5
```

```
initial
```

```
    #5 b <= a + 1;      t = 5: b assigned with 1 at the end of t = 5
```

```
module test7();
```

```
    reg [3:0] a,b;
```

```
    initial
```

```
        a=0;
```


```
    initial
```

```
        #5 a <=a+1;
```

```
    initial
```


```
        #5 b<=a+1;
```

```
endmodule
```

 


Contd...
 
```
initial
begin
a <= 0;
#20 a <= 1;
#20 b <= a + 1;
end
```


 
```
module test2();
reg a,b;
initial
begin
a<=0;
#20 a<=1;
#20 b<=a+1;
end
endmodule
```



Contd...

initial


begin

a <= 0;

#20 a <= 1;
b <= #20 a + 1;

end

 - 1) This is one 'sequential block'
- 2) All these statements will execute at time t = 20.
- 3) b will only be assigned at the end of time = 40



module test3();

reg a,b;

initial

begin

a<=0;

#20 a<=1;

b<= #20 a+1;

end

endmodule



Summary of blocking and non-blocking statements

- Commonly used to model registers in always blocks.
- Simulate the effect of multiple concurrent expressions.
- We will use non-blocking assignments to design hardware modules, FSM, data paths *etc* in a single always block.
- In practice **DO NOT MIX** non-blocking and blocking assignments in the same always block

Any Queries!



Thank you!

