

BECE102L – Digital Systems Design

Module 5 –Design of Sequential Logic Circuits

Latches, Flip-Flops - SR, D, JK & T, Buffer Registers, Shift Registers - SISO, SIPO, PISO, PIPO, Design of synchronous sequential circuits: state table and state diagrams, Design of counters: Modulo-n, Johnson, Ring, Up/Down, Asynchronous counter. Modeling of sequential logic circuits using Verilog HDL..

Dr. Rohit Mathur
Assistant Professor Sr. Grade 1
School of Electronics Engineering

flip-flop conversions

Follow these steps for converting one flip-flop to the other.

1. Consider the characteristic table of desired flip-flop.
2. Fill the excitation values inputs of given flip-flop for each combination of present state and next state.
3. Get the simplified expressions for each excitation input. If necessary, use K maps for simplifying.
4. Draw the circuit diagram of desired flip-flop according to the simplified expressions using given flip-flop and necessary logic gates.

Excitation Table for all flip-flops

Present State	Next State	SR flip-flop inputs		D flip-flop input	JK flip-flop inputs		T flip-flop input
Q_t	Q_{t+1}	S	R	D	J	K	T
0	0	0	x	0	0	x	0
0	1	1	0	1	1	x	1
1	0	0	1	0	x	1	1
1	1	x	0	1	x	0	0

SR flip-flop to D flip-flop conversion



Characteristic table of D flip-flop

D flip-flop input	Present State	Next State
D	Q_t	Q_{t+1}
0	0	0
0	1	0
1	0	1
1	1	1


Characteristic table of D flip-flop along with the **excitation inputs of SR flip-flop**.

D flip-flop input	Present State	Next State	SR flip-flop inputs	
D	Q_t	Q_{t+1}	S	R
0	0	0	0	x
0	1	0	0	1
1	0	1	1	0
1	1	1	x	0

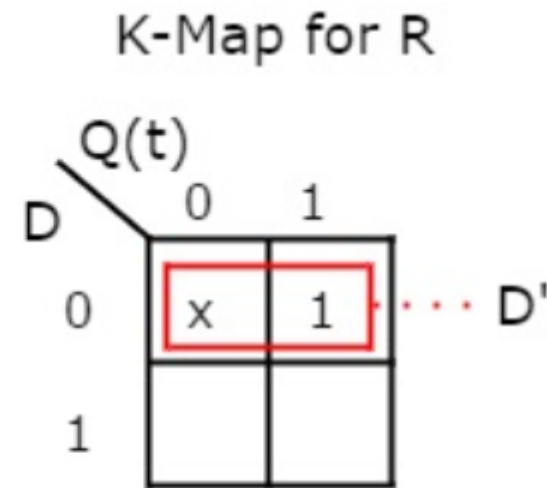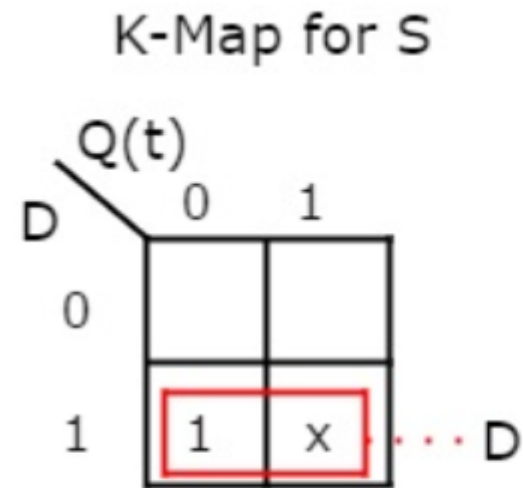We can use 2 variable K-Maps for getting simplified expressions for these inputs. The **k-Maps** for S & R are shown below.



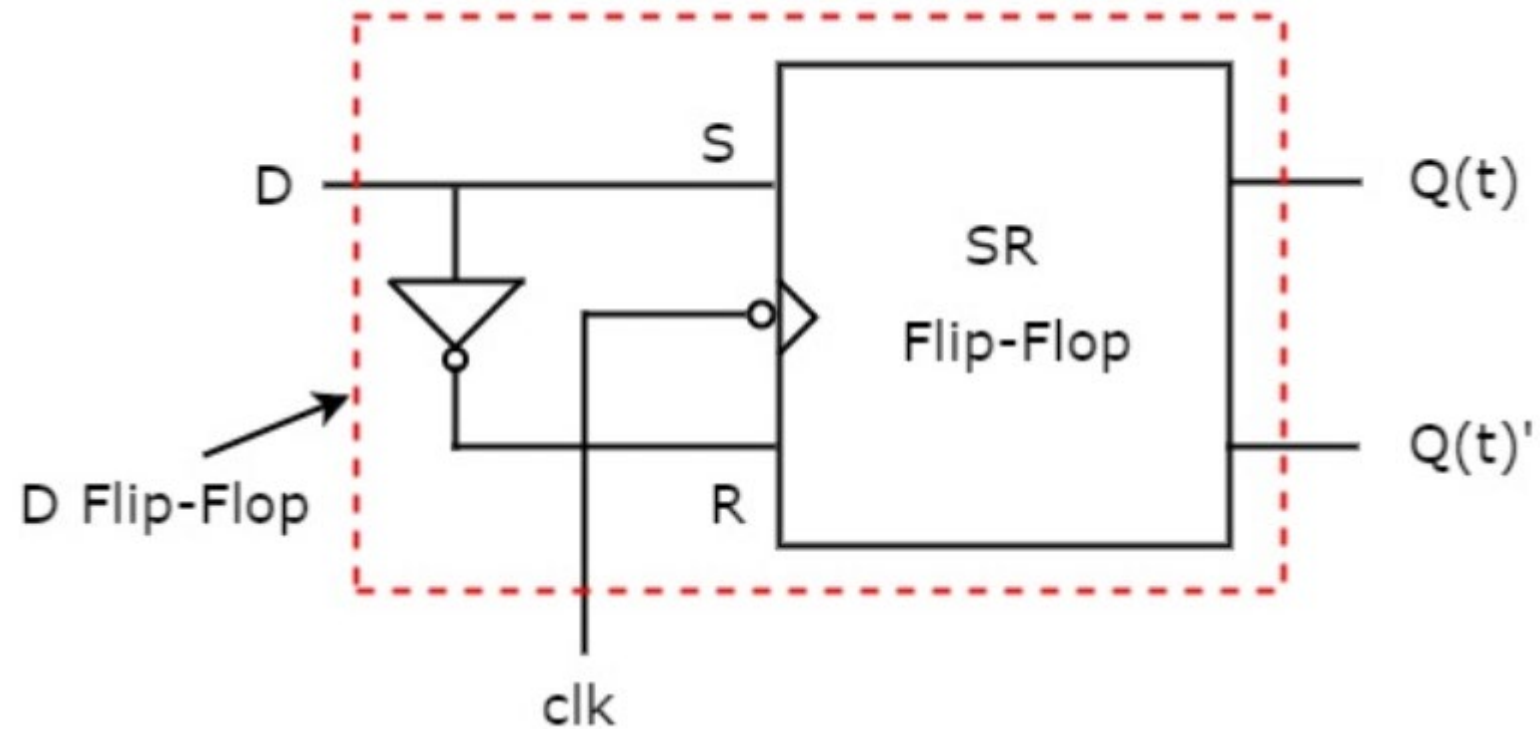So, we got $S = D$ & $R = D'$ after simplifying. The **circuit diagram** of D flip-flop is shown in the following figure.




This circuit consists of SR flip-flop and an inverter. This inverter produces an output, which is complement of input, D. So, the overall circuit has single input, D and two outputs Q_t & Q_t' .

D flip-flop to T flip-flop conversion

Characteristic table of T flip-flop along with the **excitation input of D flip-flop**

T flip-flop input	Present State	Next State	D flip-flop input
T	$Q(t)$	$Q(t+1)$	D
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

$$D = T \oplus Q(t)$$

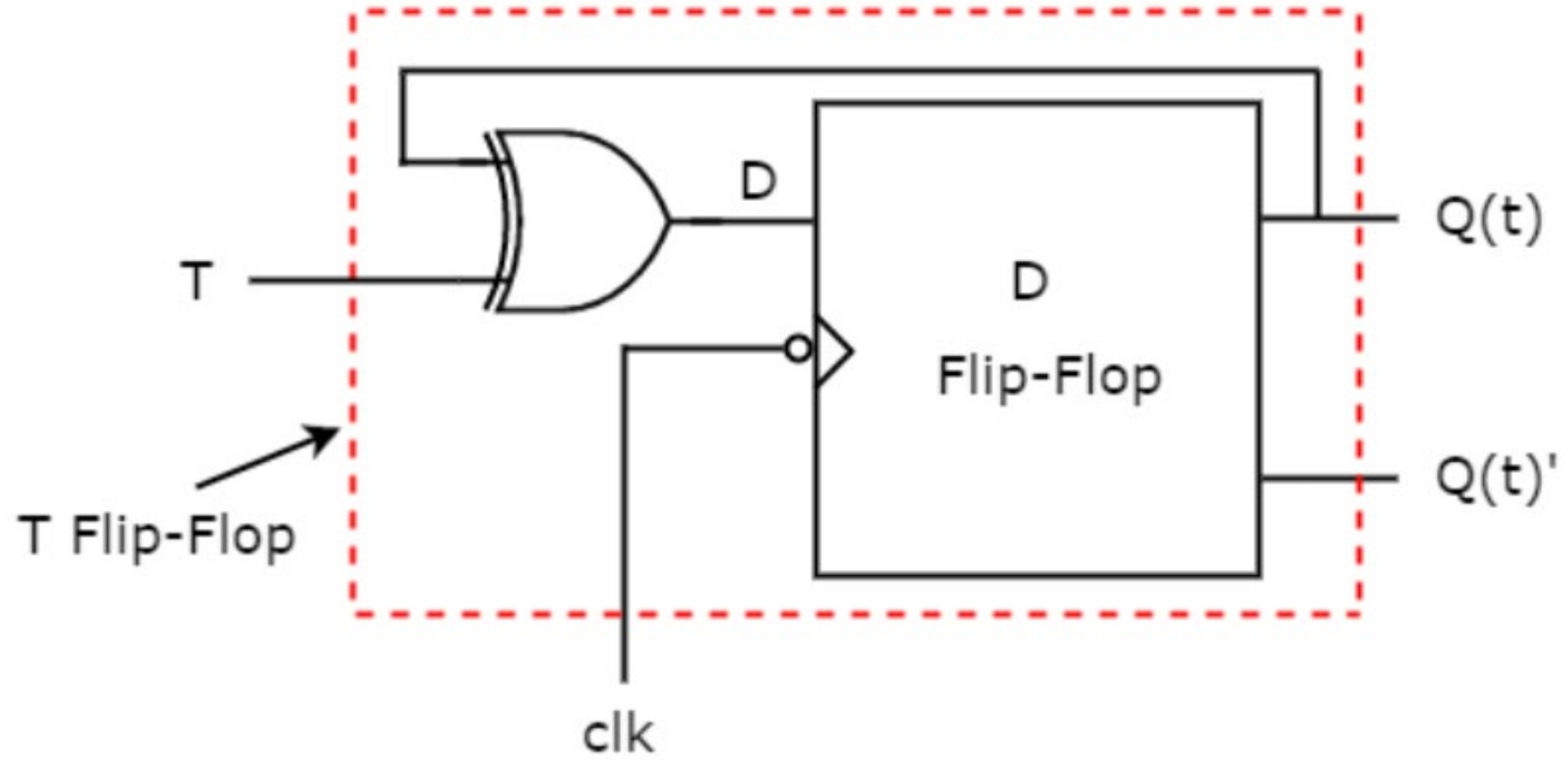

Introduction Registers

- A FF is one bit memory cell. To increase the storage capacity we use multiple FF.
- A set of n flip-flops that can be used to store n bits of information, such as an n -bit number is called as a *register*.
- A common clock is used for each flip-flop in a register.
- We know that a given number can be multiplied by 2 if its bits are shifted one bit position to the left and a 0 is inserted as the new least-significant bit.
- Similarly, the number is divided by 2 if the bits are shifted one bit-position to the right.
- These can be achieved by shifting the contents of a register.

There are four main types of shift registers:


Serial-in serial-out (SISO): The data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control.

Serial-in parallel-out (SIPO): The register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form.

Parallel-in serial-out (PISO): The parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.

Parallel-in parallel-out (PIPO): The parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.

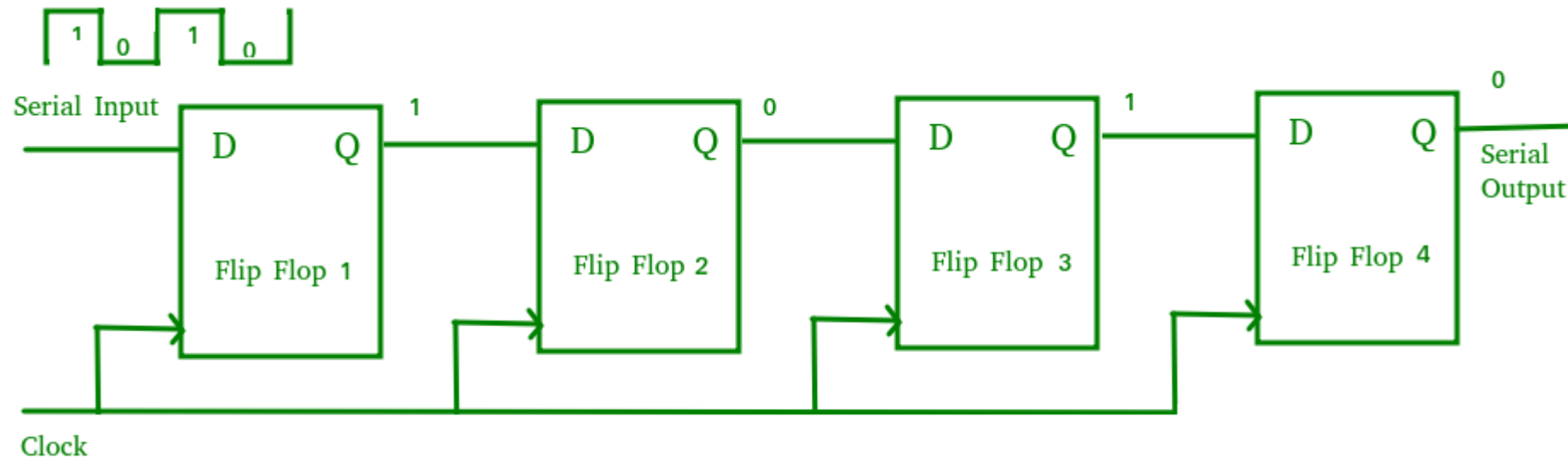
Serial In Serial Out (SISO) Shift Register




logical input 1011

Operation of the Shift-right Register					
Timing pulse	Q_A	Q_B	Q_C	Q_D	Serial output at Q_D
Initial value	0	0	0	0	0
After 1 st clock pulse	1	0	0	0	0
After 2 nd clock pulse	1	1	0	0	0
After 3 rd clock pulse	0	1	1	0	0
After 4 th clock pulse	1	0	1	1	1


1st clock pulse

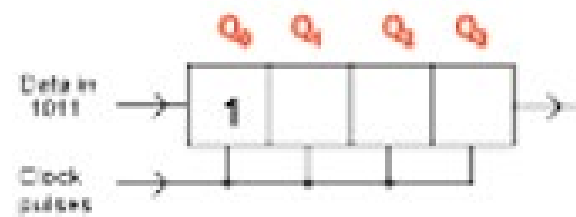


2nd clock pulse

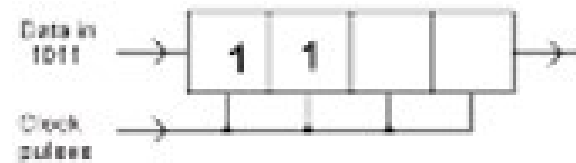


3rd clock pulse

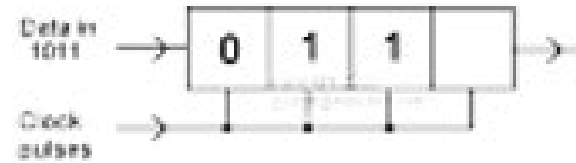

4th clock pulse

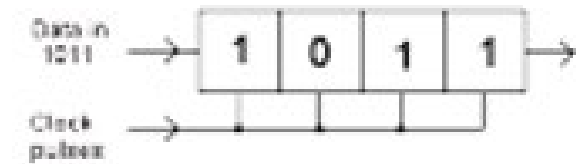


5th clock pulse

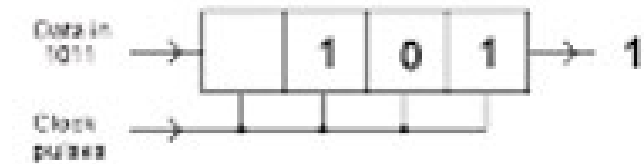


After 8th clock pulses, the register is CLEAR

Data Input

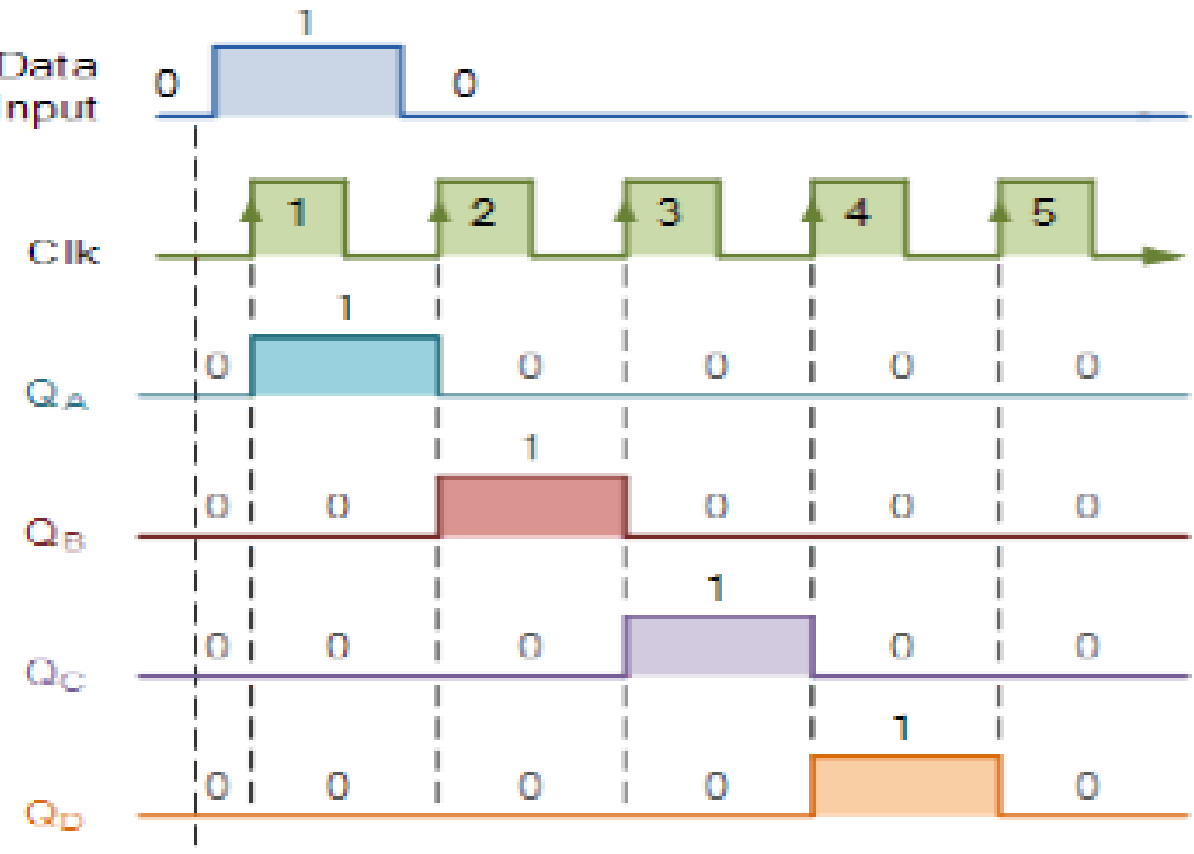


Verilog HDL – SISO (Structural Modeling)
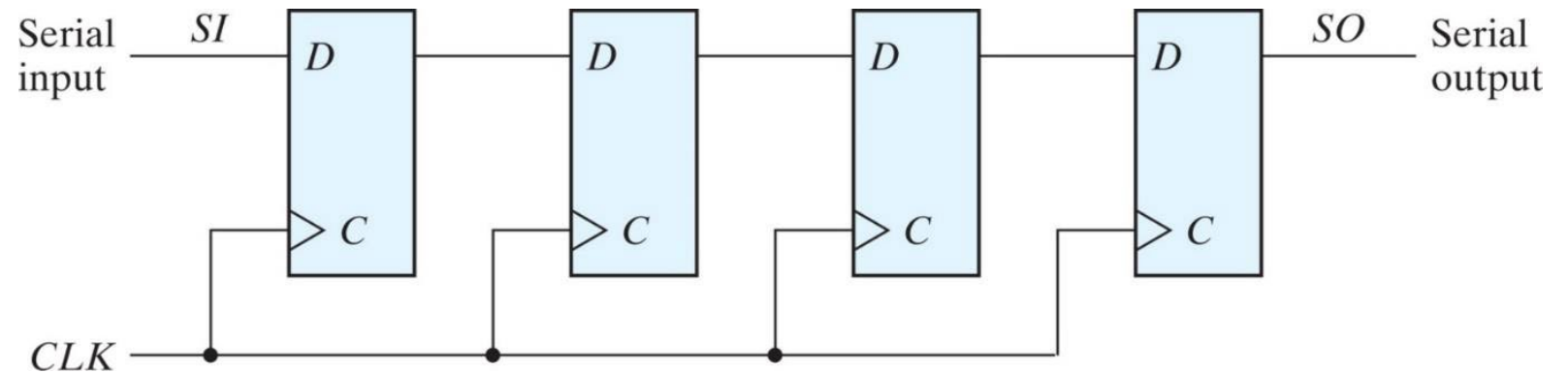
```
module siso_str(clk,si,rst,so);  
input clk,rst,si;  
output so;  
wire so;  
wire qA,qB,qC;  
dff_inst d1(clk,rst,si,qA);  
dff_inst d2(clk,rst,qA,qB);  
dff_inst d3(clk,rst,qB,qC);  
dff_inst d4(clk,rst,qC,so);  
endmodule
```




Verilog HDL – SISO (Behavioral Modeling)

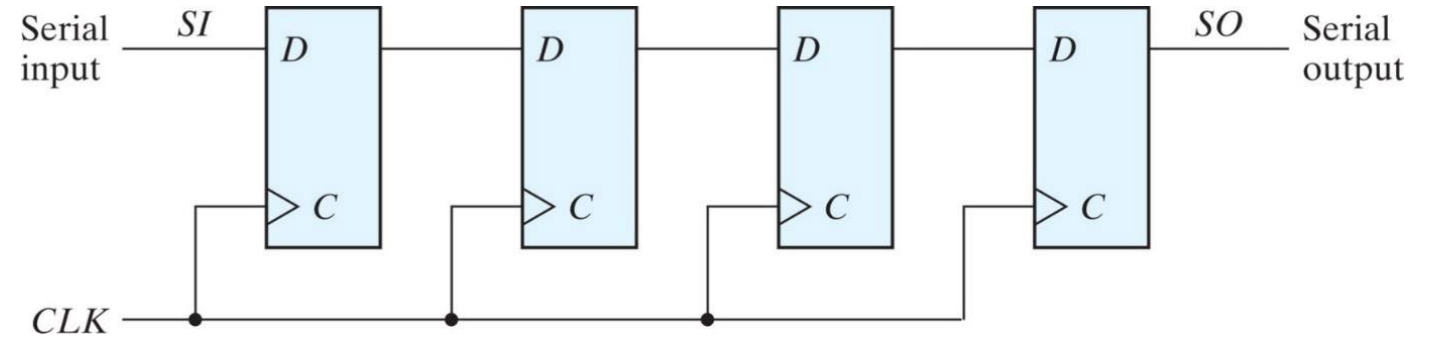
```
module siso_beh(clk,si,rst,so);  
input clk,rst,si;  
output so;  
reg qa,qb,qc,so;  
always @(posedge clk or posedge rst)  
if(rst) begin  
qa <= 1'b0; qb <= 1'b0; qc <=1'b0; so <= 1'b0;  
end  
else begin  
qa <= si; qb <= qa; qc <= qb; so <= qc;  
end  
endmodule
```



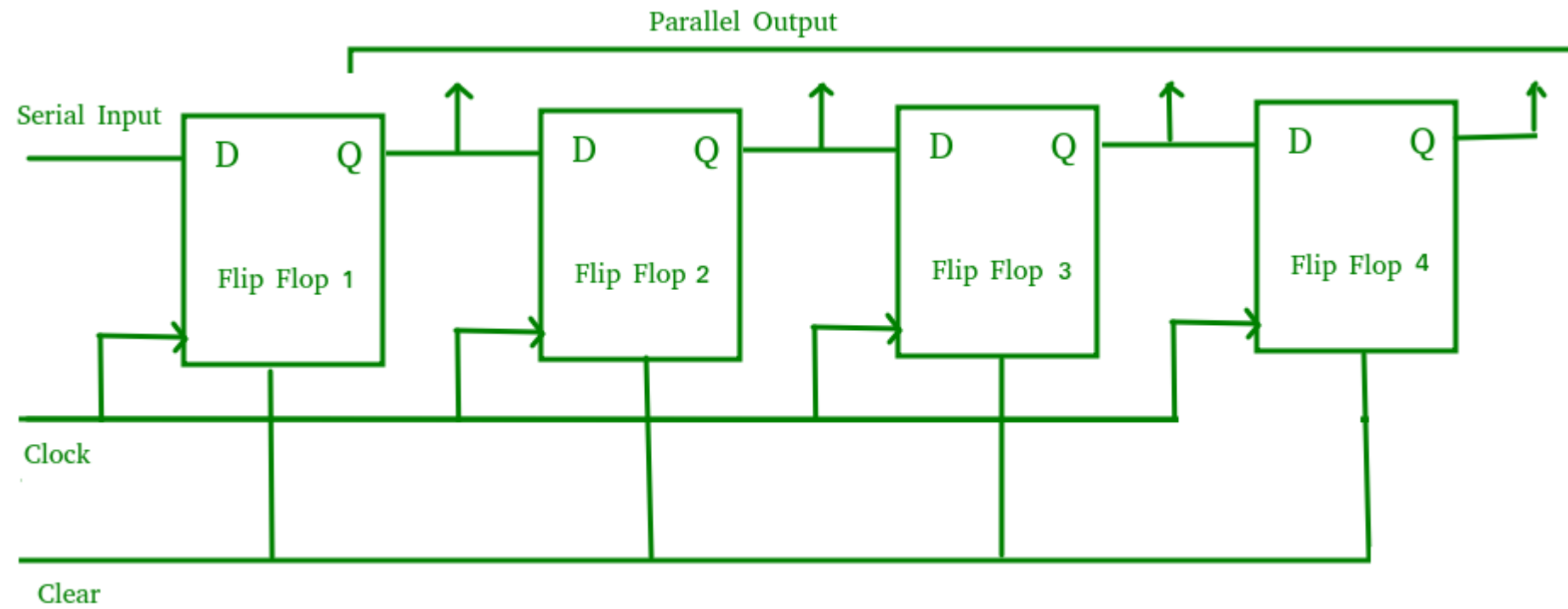
Serial In Parallel Out (SIPO) Shift Register



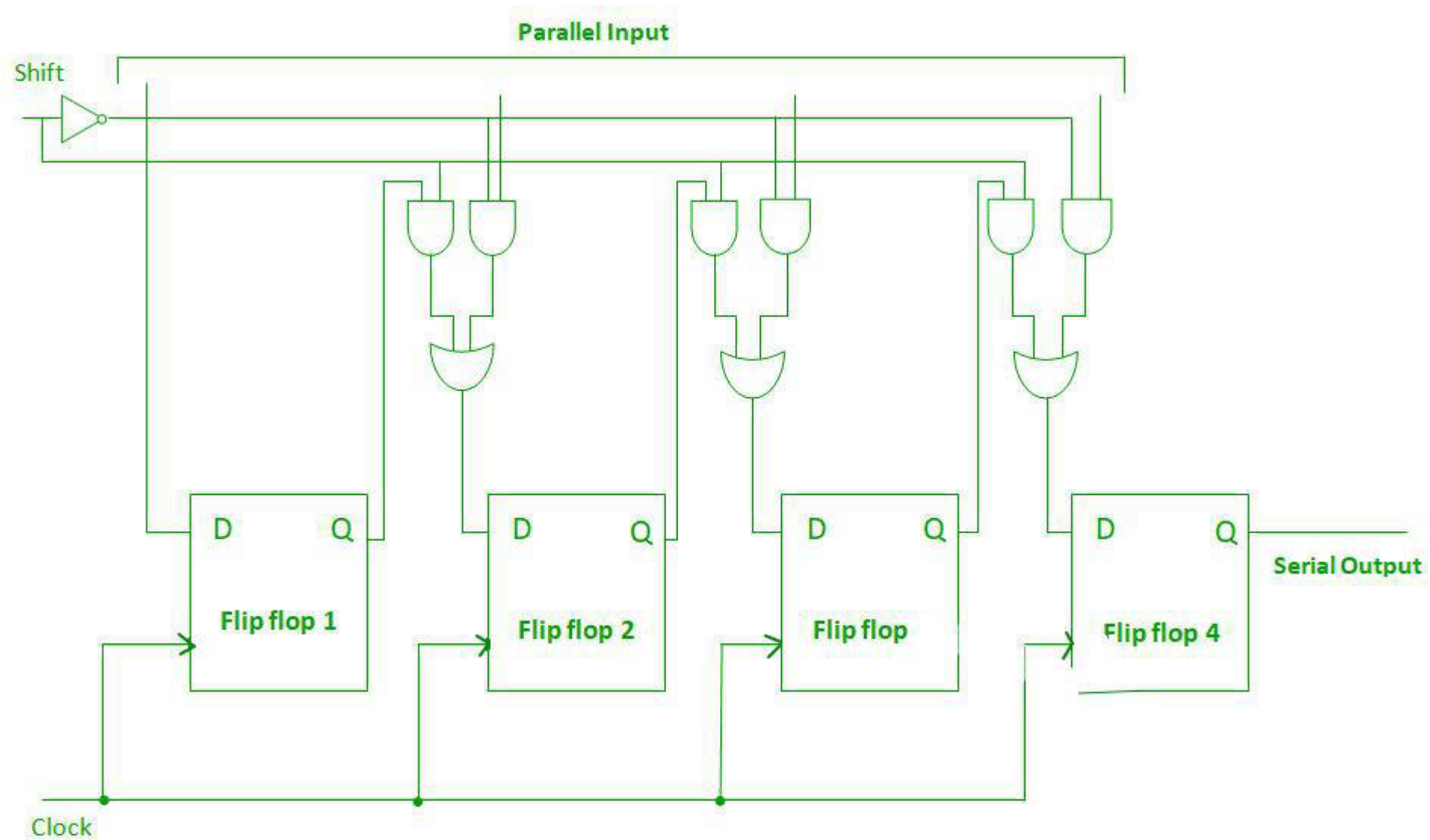Parallel In Serial Out (PISO) Shift Register




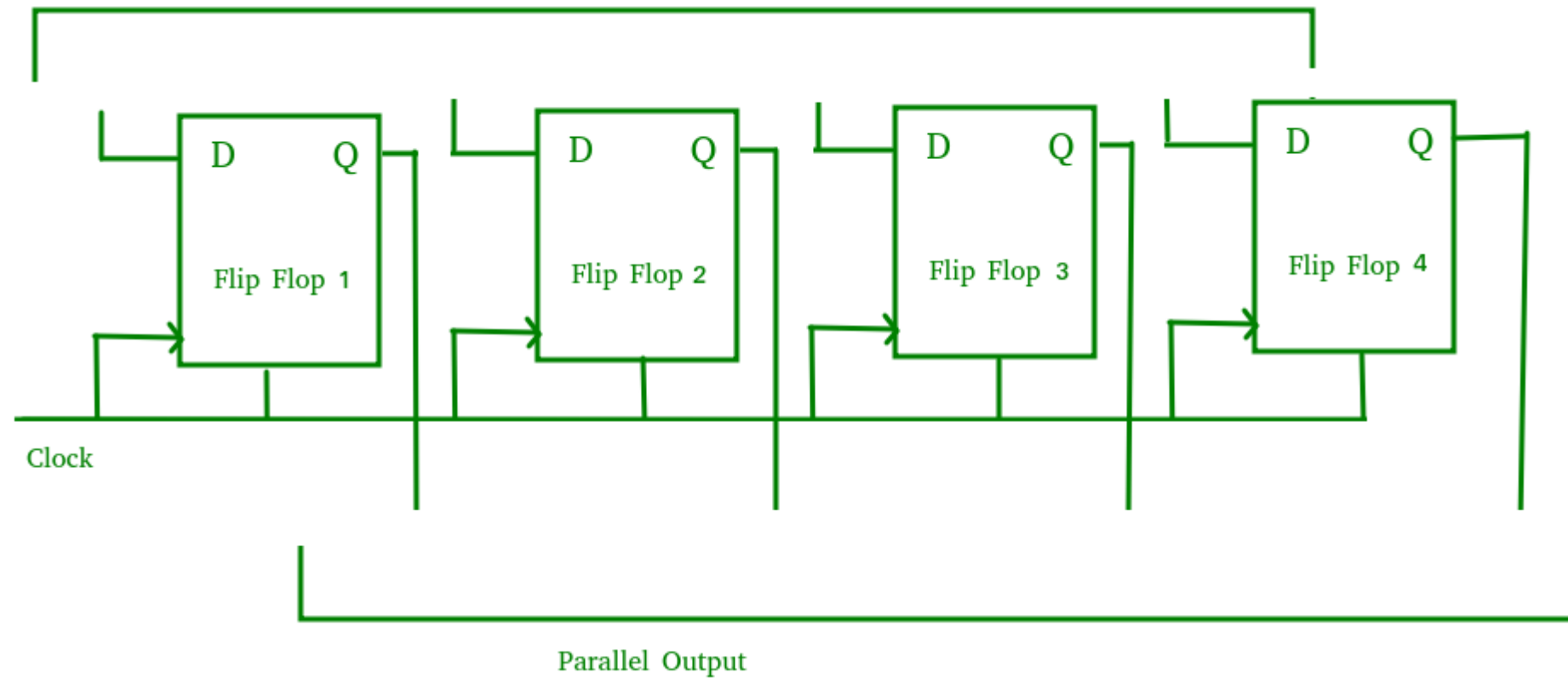Parallel In Parallel Out (PIPO) Shift Register




Counters

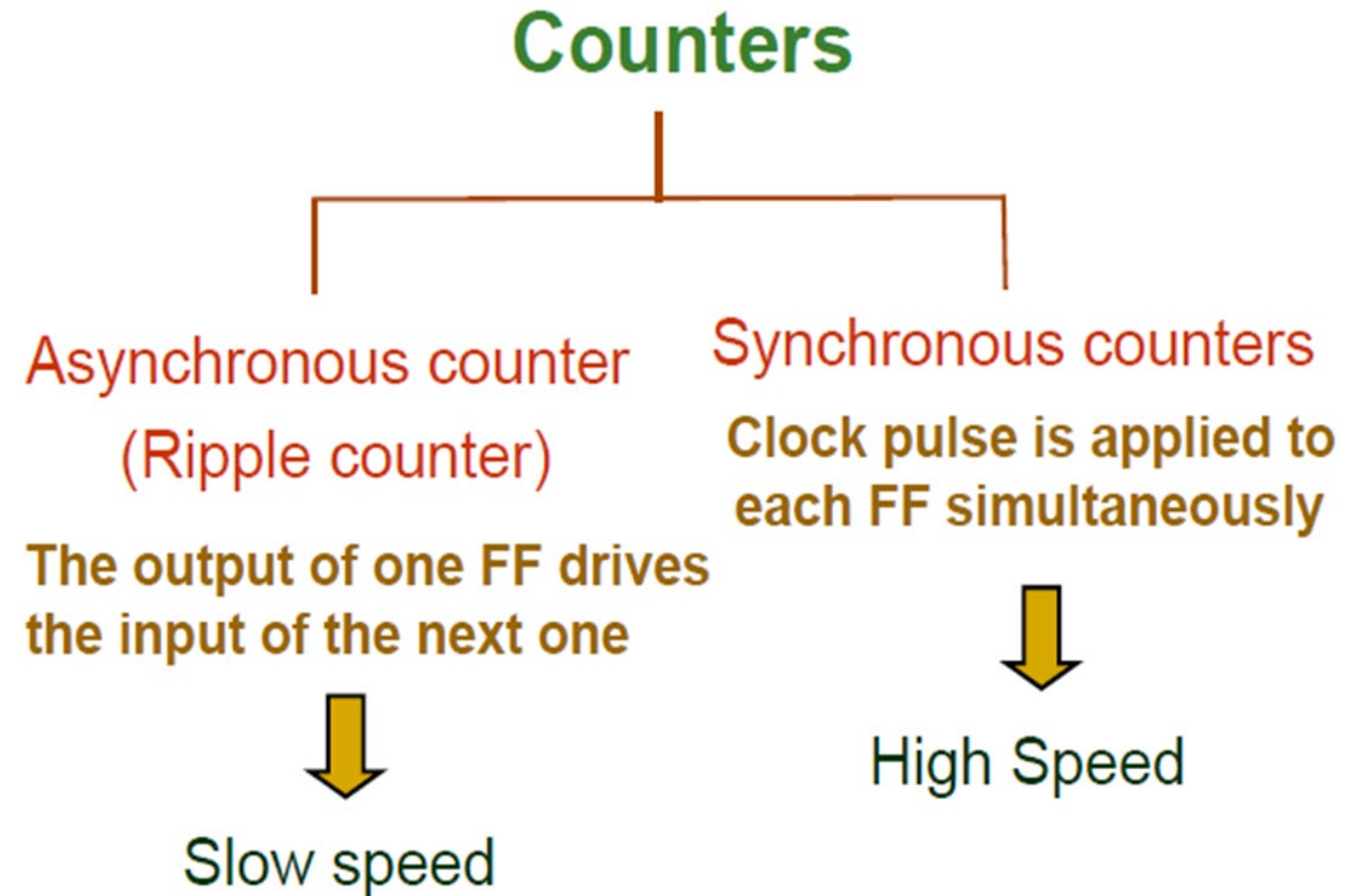- A register that goes through a prescribed sequence of states upon the application of input pulses (clock pulse) is called a counter.
1. Ripple counters - Flip flop output serves as a source for triggering other flip flops.
 2. Synchronous counters - All flip flops triggered by a single clock signal




Ring Counter

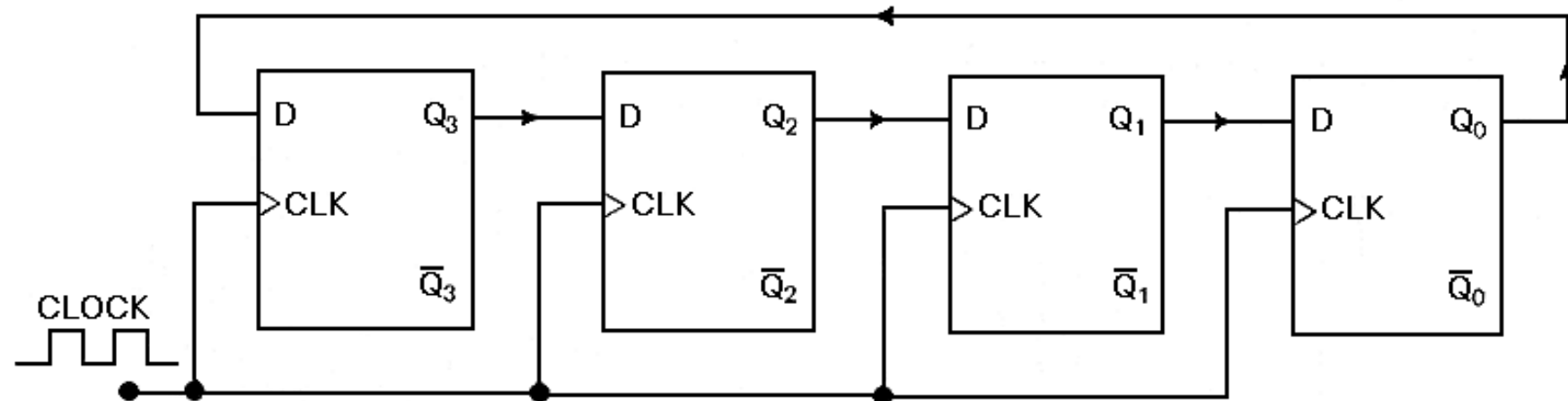- It is the special application of Shift register(circular shift register)
- The output of the last FF is given as the input of the first FF.



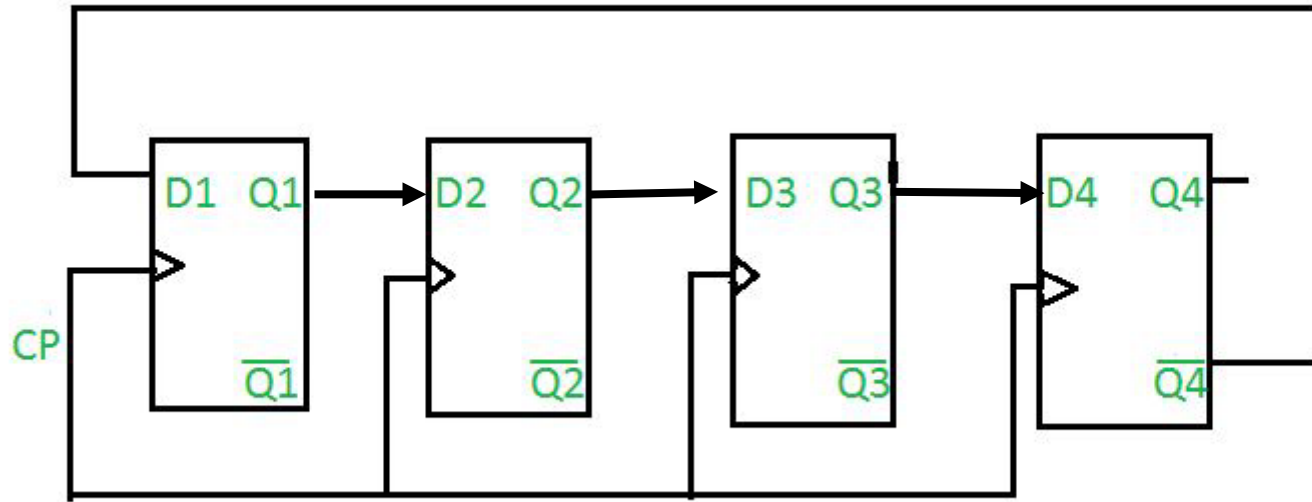Johnson counters -also known as creeping counter, is an example of synchronous counter.



CP	Q1	Q2	Q3	Q4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0