

Assesment-5 Car

Aim: To write verilog code for SR, JK, D, T, flip flop & verify it functionally


Tools Required: VSI

@Theory: SR FLIP a two-state memory circuit with set (S) & reset (R) inputs that stores a single bit of info.

Truth table:

S	R	$Q(n+1)$	State
0	0	Q_n	No change
0	1	0	RESET
1	0	1	SET
1	1	X	Invalid


Circuit Diagram

 

Ca
JK, 0, 1, flip flop

clock with set (s)
forces a single

state
change
EST
EST
valid

 

Code

```
module sr_ff (clk, rst, s, r, q);
    input clk, rst, s, r;
    output reg q;
    always @(posedg clk or posedge rst)
    begin
        if (rst == 1)
            q <= 0;
        else if (s == 0 && r == 0)
            q <= q;
        else if (s == 0 && r == 1)
            q <= 0;
        else if (s == 1 && r == 0)
            q <= 1;
        else if (s == 1 && r == 1)
            q <= ~q;
    end
endmodule
```

```
module t6();
    reg clk, rst, s, r;
    wire q;
    sr_ff uut (clk, rst, s, r, q);
    always begin
        #10 clk = ~clk;
    end
    initial
```

Op verified
25-09-2025

begin

clk = 0; cnt = 0; r = 0; s = 1;

#5 cnt = 1;

#5 cnt = 0; r = 1; s = 0;

#20 s = 1; r = 0;

#20 s = 1; r = 1;

#20 s = 0; r = 0;

#20 cnt = 1;

#5 cnt = 0;


\$ stop;

end

endmodule

JK-Flip

 theory: a type of electronic memory device that stores a single bit of information and can be used to manipulate digital data.



Truth table

J	K	Q(n+1)	State
0	0	Qn	No change
0	1	0	RESET
1	0	1	SET
1	1	Qn'	Toggle

Code

```

module jk_ff (clk, rst, j, k, q);

```

```

    input clk, rst, j, k;

```

```

    output reg q;

```

```

    always @ (posedge clk or posedge rst)
    begin

```

```

        if (rst == 1)

```

```

            q <= 0;

```

```

        else if (j == 0 && k == 0)

```

```

            q <= q;

```

```

        else if (j == 1 && k == 0)

```

```

            q <= 1;

```

```

        else if (j == 1 && k == 1)

```

```

            q <= ~q;

```

```

        end

```

```

    endmodule

```

*IP verified
 Rishy
 25-09-2025


```

module tb1;
reg clk, rst, j, k;
wire q;
jk_ff out (clk, rst, j, k, q);
always begin
# clk = 2 * clk;
end
initial
begin
clk = 0; rst = 0; j = 0; k = 0;
# 5 rst = 1;
# 5 rst = 0; j = 0; k = 0;
# 25 j = 0; k = 1;
# 25 j = 1; k = 1;
# 25 j = 1; k = 0;
# 5 rst = 1;
# 25 rst = 0; j = 1; k = 1;
$stop;
end
endmodule

```

theory:

Circuit

1-

u

~~25~~

For

m

i


e

c

T flip flop

theory: a digital electronic circuit with a single input (T) that changes its output state (Q) when enabled. clock pulse with T to high and maintain its current state when T to low

Circuit

 

Truth table

T	Q(n+1)	State
0	Q	No change
1	Q'	Toggle

Code

```
module t_ff (clk, rst, t, q);  
  input clk, rst, t;  
  output reg q;  
  always @(posedge clk or posedge rst)  
  begin  
    if (rst == 1)  
      q <= 0;  
    else if (t == 1)  
      q <= ~q;  
    else  
      q <= q;  
  end  
end
```



```

module tb1;
  reg clk, rst, t;
  wire q;
  b-hw (clk, rst, bqr);
  always begin
    #10 clk = ~clk;
    end
  initial
    begin
      clk = 0; rst = 0; t = 0;
      #5 rst = 1;
      #10 t = 0;
      #15 t = 1;
      #20 rst = 1;
      #25 rst = 0; t = 1;
      $stop;
    end
endmodule

```

Theory: a
stor
a d
imp
d


Circuit

Tr

D flip flop

Theory: a clock sequential logic circuit - that stores a single bit of binary data, acting as a delay element by copying its data (b) input to its output (Q) at the moment of a clock edge.

Circuit:

 

Truth-Table

D	Q (next)	State
0	0	RESET
1	1	SET

Code:

```
module dff (clk, rst, d, q);  
    input clk, rst, d;  
    output reg q;  
    always @ (posedge clk or posedge rst)  
    begin  
        if (rst == 1)  
            q <= 0;  
        else  
            q <= d; end endmodule
```

O/p Verified
Date
25-09-2025


```

module tb1;
  reg clk, rst, d;
  wire q;
  dff q1 (clk, rst, d, q);
  always begin
    #10 clk = ~clk;
  end
  initial
  begin
    #5 clk = 0, rst = 0, d = 0;
    #5 rst = 1;
    #5 rst = 0, d = 0;
    #15 d = 1;
    #10 d = 0;
    #15 d = 1;
    #5 rst = 1;
    #5 rst = 0, d = 1;
    $stop;
  end
endmodule

```


Assessment - S(ub)

Aim: To write the verilog Code for SISO
SISO shift register

Tools Required: VSIM


Theory:

SISO: fundamental sequential digital logic circuits that shift data bit-by-bit, controlled by a clock signal

SISO: a shift register also uses a series of interconnected flip-flops, but each flip-flop's output is accessible as a separate parallel output

Circuit Diagram

SISO

 

S2PO



Truth table:

S2PO

CLK	'Q3'	'Q2'	'Q1'	'Q0'
1st	0	0	0	0
2nd	1	0	0	0
3rd	1	1	0	0
4th	1	1	1	0

S2PO

Clock	Q1	Q2	Q3	Q4
0	1	0	0	1
1	1	1	0	0
2	0	1	1	0
3	0	0	1	1

Code

```
module SISO (o0, si, clk, rst);
```

```
output o0;
```

```
input si, clk, rst;
```

```
reg [3:0] q;
```

```
always @ (posedge clk or posedge rst)
```

```
begin
```

```
if (rst)
```

```
q <= 4'b0;
```

```
else
```

```
q <= {0, q[3:1]};
```

```
end
```

```
assign s = q[0]
```

```
endmodule
```

```
module student ()
```

```
begin
```

```
wire o0;
```

```
reg si, clk, rst;
```

```
si <= 0
```

```
o0 (<= o0, si, clk, rst);
```

```
always
```

```
# 5 clk = ~clk;
```

```
initial begin
```

```
si <= 0; clk <= 0; rst <= 1;
```

```
# 10 rst <= 0;
```

```
si <= 1;
```



```

# 10 q1 = 0;
# 10 q1 = 0;
# 10 q1 = 1;
# 10 q1 = 1;
# 50 $stop;
end
endmodule

```

Code

```

module sipo(q, si, clk, rst);
    output [3:0] q;
    input si, clk, rst;
    reg [3:0] q;
    always @ (posedg clk or posedge rst)
    begin
        if (rst)
            q <= 4'b0;
        else
            q <= {q1, q[3:1]};
    end
endmodule

```

```

module sipo_tb;
    wire [3:0] q;
    reg si, clk, rst;
    sipo el(q, si, clk, rst);
    always
    # 5 clk = ~clk;

```


initial
regin

ar = 0;

clk = 0;

out = 1;

#10 out = 0;

#100 = 1;

#10 ar = 0;

#10 ar = 0;

#10 ar = 1;

#10 ar = 0;

#10 ar = 1;

#50 \$stop;

end

endmodule

011
944
301111
248 000005 944

Conclusion

The verilog code is successfully unified

Assessment - 1st

Aim - To verify verilog code for up-down counter
(b) Module N-count (n=10)
(c) Johnson counter

Tools Required: Modelsim


Theory - UP-down Counter: A counter that can go from 0 to count in either an ascending or descending order based on a control signal. It increases from a low value to a high value or decreases from a high value to a low value.

Module-n-Counter: A counter with a specific number of unique states, denoted by 'n'. It starts from 0 to $n-1$ & then resets, having a total of n unique states.


Johnson Counter: A counter where the inverted output of the last flip-flop is connected to the input of the first flip-flop. This creates a sequence of states that is twice the number of flip-flops. For example, a 3-stage Johnson counter has a modulus of 6.

Circuit Diagram

UP-down

 

Module-n counter

 


Johnson




Circuit Diagram


UP-down

 

modulo-n counter

 

Johnson Counter

 

Q code

```
module up-down (Q, up-down, clk, rst);  
    Output [3:0] Q;  
    input up-down, clk, rst;  
    reg [3:0] Q;  
    always @ (posedg clk or posdeg rst);  
    begin  
        if (rst)  
            Q <= 4'b0;  
        else if (up-down)  
            Q <= Q + 1;  
        else  
            Q <= Q - 1;  
        end  
    endmodule
```

0 1 2 999 1000

```
module up-down-test;  
    wire [3:0] Q;  
    reg up-down, clk, rst;  
    up-down ud1 (Q, up-down, clk, rst);  
    always  
        # 5 clk = ~clk;
```

initial

begin

(clk = 0) up-down = 1; rst = 1;

10 rst = 0;

100 up-down = 0;

200 \$stop;

end
endmodule

b) Code

```
module modN_counter (O, clk, rst);  
    output [3:0] O;  
    input  clk, rst;  
    reg [3:0] O;  
    always @(posedge clk or posedge rst);
```

```
begin  
    if (rst)  
        O <= 4'b0;  
    else if (O == 9)  
        O <= 4'b0;  
    else  
        O <= O + 1;  
    end  
endmodule
```

```
module modN_counter_tb;  
    wire [3:0] O;  
    reg clk, rst;  
    modN_counter mcb (O, clk, rst);  
    always
```

```
#5 clk = ~clk; //  
initial  
begin  
    clk = 0; rst = 1;  
#10 rst = 0;  
#200 $stop;
```

200ns
30ns
200ns 0.805

end
endmodule

(C) Johnson Counter

```
module johnson_counter (q, clk, reset);  
    output [3:0] q;  
    input clk, rst;  
    reg [3:0] q;  
    always @(posedg clk or posedge rst)
```

```
begin  
    if (rst)  
        q <= 4'b0000;  
    else  
        q <= {~q[0], q[3:1]};  
    end  
endmodule
```

O/P verified
Silly
30-10-2025

```
module johnson_counter_tb;
```

```
    wire [3:0] q;
```

```
    reg clk, rst;
```

```
    johnson_counter j1 (q, clk, rst);
```

```
    always
```

```
    # 5 clk = ~clk;
```

```
    initial
```

```
    begin
```


```
        clk <= 0; rst <= 1;
```

```
        # 10 rst <= 0;
```

```
        # 200 $stop;
```

```
    end
```

```
endmodule
```

 Activities MTIDialog

ModelSim - INTEL FPGA STARTER EDITION 2020.1

File Edit View Compile Simulate Add Wave Tools Layout Bookmarks Window Help

Calculator

1 0 10 11 12

Search

Search

Instance	Design unit	Design unit type	Top Category	Visibility	Total coverage
tb_jk	tb_jk	Module	DU Instance	+acc=cl...	
jk_tf	jk_tf	Module	DU Instance	+acc=cl...	
#ALWAYS#24	tb_jk	Process	-	+acc=cl...	
#INITIAL#27	tb_jk	Process	-	+acc=cl...	
evsim_capacity#	Capacity	Statistics	-	+acc=cl...	


Name	Value	Kind	Mode
clk	1	Regis... Internal	
j	0	Regis... Internal	
k	1	Regis... Internal	
q	S10	Net Internal	
rst	0	Regis... Internal	



Project: hg

Now: 100 ps Delta: 2

sim/tb_jk

 

activities MtiDialog

Sep 18 1:00 PM

ModelSim - INTEL FPGA STARTER EDITION 2020.1


Edit View Compile Simulate Add Wave Tools Layout Bookmarks Window Help

Layout Simulate

ColumnLayout Default

Instance	Design unit	Design unit type	Top Category	Visibility
tb_d	tb_d	Module	DU Instance	+acc=<f
uut	d_ff	Module	DU Instance	+acc=<f
#ALWAYS#18	tb_d	Process	-	+acc=<f
#INITIAL#21	tb_d	Process	-	+acc=<f
#vsim_capacity#		Capacity	Statistics	+acc=<f


Name	Value	Kind	Mode
rst	0	Regi...	Internal
q	St1	Net	Internal
d	1	Regi...	Internal
clk	1	Regi...	Internal

 

```


# Loading work.tb_d
# Loading work.d_ff
add wave -position insertpoint \
sim:/tb_d/rst \
sim:/tb_d/q \
sim:/tb_d/d \
sim:/tb_d/clk \
VSIM 34> run
# Note: Sstop : /home/matlab/downloads/24bce0837/dflplop.v(32)
# Time: 65 ps Iteration: 0 Instance: /tb_d
# Break in Module tb_d at /home/matlab/downloads/24bce0837/dflplop.v line 32
VSIM 35>
0 ps to 126 ps
Project: rush Now: 65 ps Delta: 0

```

 


sim - Default	Design unit	Design unit type	Top Category	Visibility
Instance				
tb_d	tb_d	Module	DU Instance	+acc=<l
uut	d_ff	Module	DU Instance	+acc=<l
#ALWAYS#18	tb_d	Process	-	+acc=<l
#INITIAL#21	tb_d	Process	-	+acc=<l
#vsim_capacity#		Capacity	Statistics	+acc=<l



Objects	Name	Value	Kind	Mode
	rst	0	Regi...	Internal
	q	St1	Net	Internal
	d	1	Regi...	Internal
	clk	1	Regi...	Internal

 


```
Transcript
# Loading work.tb_d
# Loading work.d ff
add wave -position insertpoint \
sim:/tb_d/rst \
sim:/tb_d/q \
sim:/tb_d/d \
sim:/tb_d/clk
VSI3M 34> run
** Note: Sstop : /home/matlab/downloads/24bce0837/dflipflop.v(32)
Time: 65 ps Iteration: 0 Instance: /tb_d
# Break in Module tb_d at /home/matlab/downloads/24bce0837/dflipflop.v line 32
VSI3M 35>
```

 Project : rush Now: 65 ps Delta: 0 /tb_d/clk
0 ps to 126 ps



  

 

Activities

WindowObj

Oct 30 12:18 PM

Wave

File Edit View Add Format Tools Bookmarks Window Help

Wave - Default



Search:



Msgs

1001



/up_down_test/Q

1



/up_down_test/up_down

0




/up_down_test/clk

0



/up_down_test/rst

0

 


Now 100 ps

Cursor 1 0 ps

0 ps to 178 ps

Now: 100 ps Delta: 2

 

Activities WindowObj

Oct 30 12:57 PM

Wave

File Edit View Add Format Tools Bookmarks Window Help

Wave - Default

Search

	Msps
/seq_mealy_test/y	S10
/seq_mealy_test/i	0
/seq_mealy_test/clk	0
/seq_mealy_test/rst	0

